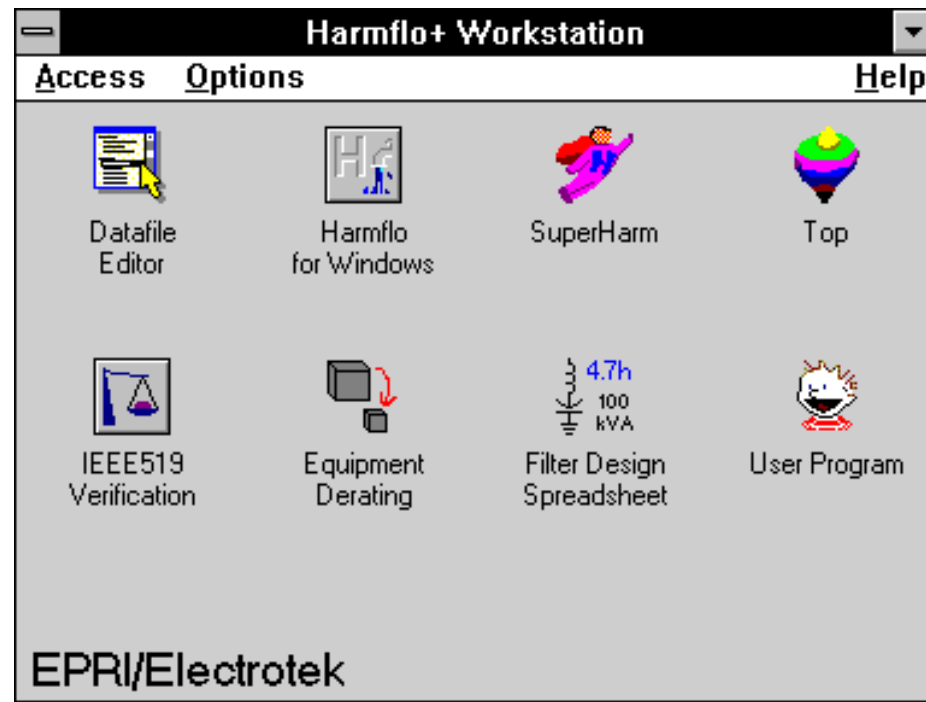


Harmonic Analysis

Using the HarmFlo+ Workstation



HarmFlo+ Case Study Workshop
Modeling and Analysis of Adjustable-Speed Drives
October, 1993

Overview


- ❑ Introduction to Power Electronics Modeling
- ❑ Modeling Considerations
- ❑ Development of SuperHarm Models
- ❑ Harmonic Aspects of ASD Applications
- ❑ ASD Case studies

DC Motors

- ❑ Advantages:
 - Variable characteristics
 - Extensively used in variable-speed drives
 - A high starting torque
 - A wide range of speed control
 - Simpler and less expensive speed control
- ❑ Disadvantages:
 - Needs commutators
 - Costs more
 - Needs more maintenance
 - Not suitable for very high speed applications

DC Motors

□ Basic Characteristics of DC Motors

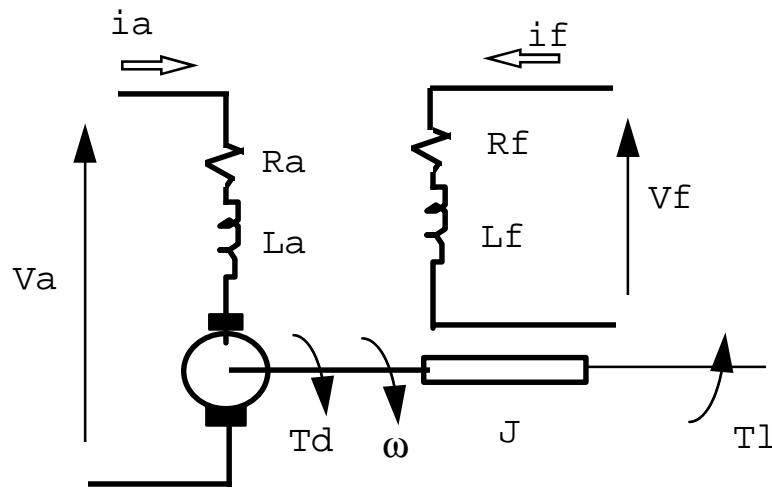

$$V_f = R_f i_f + L_f \frac{di_f}{dt}$$

$$V_a = R_a i_a + L_a \frac{di_a}{dt} + e_g$$

$$e_g = K_v \omega i_f$$

$$T_d = K_t i_f i_a$$

$$T_d = J \frac{d\omega}{dt} + B\omega + T_L$$

Under steady state: $P_d = T_d \omega$

DC Motors

$$\mathbf{W} = \frac{V_a - R_a I_a}{K_v \frac{V_f}{R_f}}$$

for parallel excitation,


$$\mathbf{W} = \frac{V_a - R_a I_a}{K_v I_a}$$

for series excitation


DC Motor speed can be controlled by :

- Voltage control, controlling V_a ,
- Field control, controlling I_f , and
- Torque demand control, controlling I_a for a fixed I_f

DC Motors

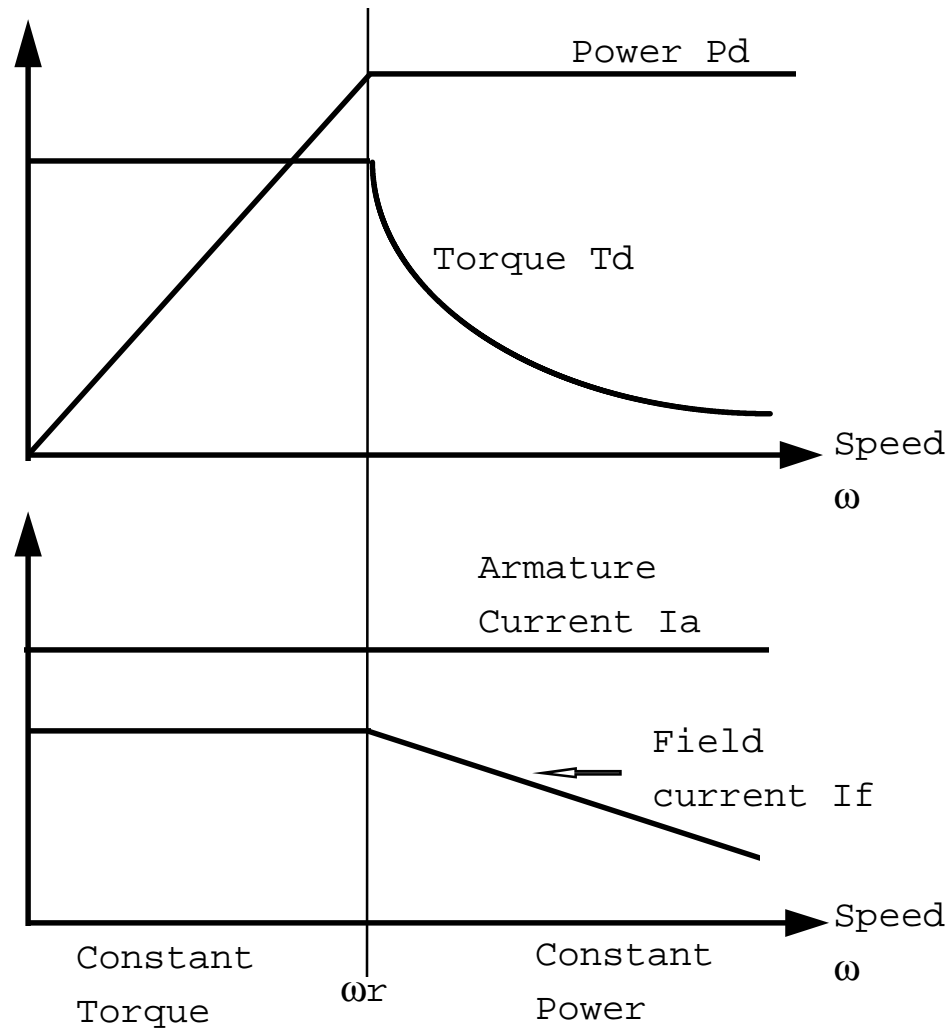

DC Motors

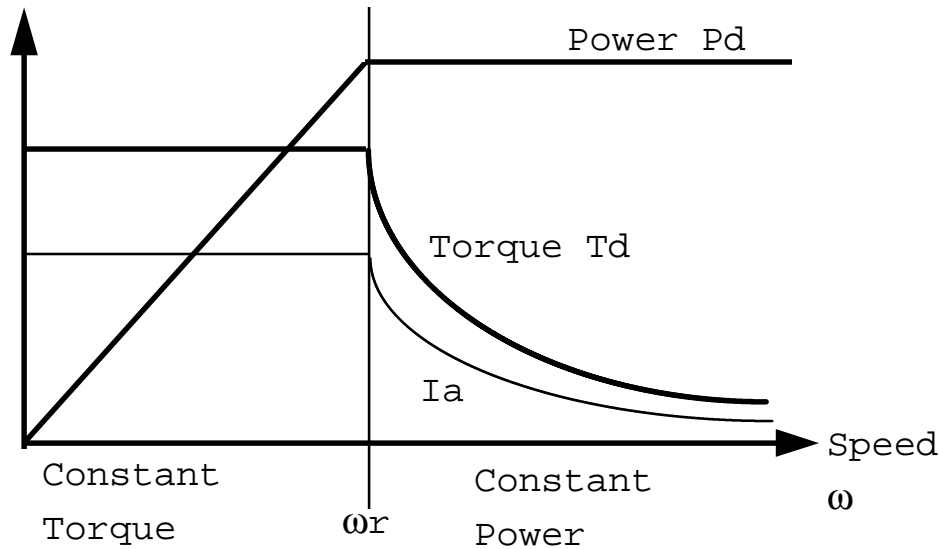

For this parallel excited dc motor, in practice, according to the speed range, two control methods are used.

When $\omega < \omega_r$, I_a and I_f are maintained constant ω is changed by varying V_a for a constant torque.

When $\omega > \omega_r$, V_a is maintained at the rated value and the I_f is varied to control the speed for a constant power.

DC Drives

- Generally, DC drives can be classified into three types:
 - Single-phase drives
 - » Semiconverter drives
 - » Full-converter drives
 - Three-phase drives
 - » Semiconverter drives
 - » Full-converter drives
 - Chopper drives
 - » A dc chopper is connected between a fixed-voltage dc source and dc motor to vary the armature voltage.

AC Motors

- ❑ AC motor advantages
 - Lightweight (20 to 40 % lighter than dc motor)
 - Inexpensive
 - Low maintenance
 - High speed operation

- ❑ Disadvantages
 - Expensive drive
 - Complex control
 - » need sensors, or
 - » vector control

AC Motor Drives

- ❑ AC drives can be
 - Synchronous motor drives
 - Induction motor drives

- ❑ Basic structure
 - AC input-to-DC link-to-AC output

- ❑ Classified by DC link types
 - Voltage source inverter (VSI)
 - Current source inverter (CSI)

AC Motor Drives

□ Controls

Through controlling power converters, inverters, and ac voltage controllers, frequency, voltage/current for variable speed applications can be obtained.

- Stator voltage control
- Rotor voltage control
- Frequency control
- Stator voltage and frequency control
- Stator current control
- Voltage, current, and frequency control

Three-Phase vs. Single-Phase Models

- ❑ Single-phase models (positive sequence) for balanced loads, balanced system, balanced harmonic generation
- ❑ Separate solution for zero sequence harmonics
- ❑ System unbalances, harmonic source unbalances may require a three phase model

When is a Current Source Model Valid?

- ❑ Valid for conditions where the system impedance is much smaller than the internal impedance of the harmonic source.
- ❑ Not valid when the system approaches resonance (high impedance) ($V_{\text{THD}} > 10\%$)
- ❑ Some loads look like a voltage source behind a high impedance (arc furnace, fluorescent lighting)

Role of Measurements

- ❑ Determine harmonic source characteristics
 - Waveform
 - Spectrum

- ❑ Verify harmonic simulation model
 - Use current spectrum from measurement
 - Compare simulated and measured voltage distortion levels

- ❑ Statistical Characteristics

Integrating Field Measurements

- Characterizing Harmonic Sources
 - Correcting phase angles
 - Lumping sources
 - SuperHarm harmonic source models

- Verifying the system model

Are Phase Angles Necessary?

- ❑ System with only one harmonic source
 - NO (unless plotting waveform is desired)

- ❑ System with multiple harmonic sources - may not be necessary if:
 - Harmonic sources are similar (little cancellation of harmonic currents)

Phase Angle Correction

When measured harmonic spectrum is based on a cosine series:

$$\Theta_{h_{\text{sim}}} = \Theta_{h_{\text{measured}}} + (h - 1) * 90^\circ$$

Sin series:


SuperHarm, V-HARM, HARMFLO 5.0

Cos series:

EMTP

Lumped Harmonic Sources

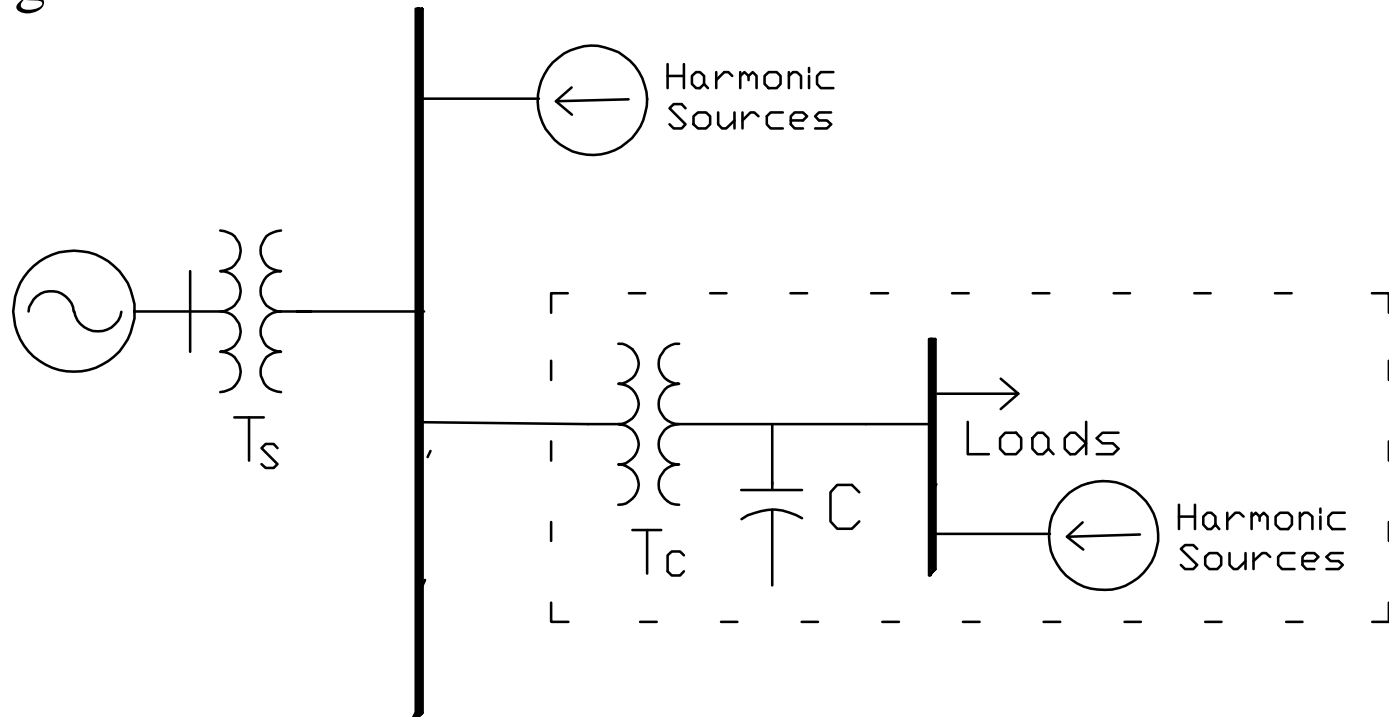Can the customer harmonic injection be represented as a single harmonic current source at point of common coupling?



SuperHarm Data Preparation

- ❑ Node Names
- ❑ Tagged Fields, Lists, and Tables
- ❑ Device Library
- ❑ Directives

SuperHarm Data Preparation - cont

Device and Node Names:

Case not important “A” = “a”

_ (underscore) is valid character

Eight (8) characters or less

Convention six (6) characters plus .A, .B, .C

Example: SrcBus.A SrcBus.B SrcBus.C

SuperHarm Data Preparation - cont

Tables:

- Tables: list of items, where each item is a list

Example:

```
TABLE = {
  { 1, 100.0, -75.0},
  { 5, 33.6, 156.0},
  { 7, 1.6, -151.0},
  {11, 8.7, -131.0},
  {13, 1.2, 54.0},
  {17, 4.5, -57.0},
  {19, 1.3, -226.0},
  {23, 2.7, 17.0},
  {25, 1.2, -149.0}
}
```

SuperHarm Data Preparation - cont

SuperHarm Device Library:

- ❑ BRANCH Single-phase R-X
- ❑ BRANCH3 Three-phase R-X (sequence quantities)
- ❑ CAPACITOR Single or three-phase capacitor
- ❑ LINEARLOAD Single-phase load
- ❑ NONLINEARLOAD Single-phase current source
- ❑ SERIESFILTER Single-phase L-C
- ❑ TRANSFORMER Single or three-phase transformer bank
- ❑ VSOURCE Single-phase voltage source

SuperHarm Data Preparation - cont

SuperHarm Device: **BRANCH**

- Example: Branch from BUS1A to BUS2A with
 $Z = 5 \Omega @ 75^\circ$

```
// Single-phase branch, Z = 5 ohms
```

```
BRANCH                      Name = B1  
                                    From = BUS1A                      To = BUS2A  
                                    R = 1.29                                      X = 4.83
```


SuperHarm Data Preparation - cont

SuperHarm Device: **BRANCH3**

- Example: 115kV source equivalent @ bus SRC1?
 $Z_1 = 0.08 + j 0.50 \% @ 10 \text{ MVA}$
 $Z_0 = 0.04 + j 0.24 \% @ 10 \text{ MVA}$

```
// Three-phase source equivalent  
  
BRANCH3            Name = SRC1  
                    From.A = V115A            To.A = SRC1A  
                    From.B = V115B            To.B = SRC1B  
                    From.C = V115C            To.C = SRC1C  
                    R1 = 1.10                 X1 = 6.63  
                    R0 = 0.52                 X0 = 3.11
```

SuperHarm Data Preparation - cont

SuperHarm Device: **CAPACITOR**

- Example: 34.5kV, 9.0 MVAr capacitor bank (wye-gnd)
 @ bus CAP1_A

```
// Three-phase capacitor bank

CAPACITOR      Name = CAP1
                  Bus.A = CAP1_A                   Bus.B = CAP1_B
                  Bus.C = CAP1_C                   Neutral = Ground
                  kV = 34.5                        MVA = 9.0
```

SuperHarm Data Preparation - cont

SuperHarm Device: **LINEARLOAD**

- Example: 480 Volt, 800 kVA, $\text{dpf} = 85\%$ served by:
1000kVA Xfmr, 4.16kV /480V, $Z_{\text{tx}} = 6\%$
@ bus 4160_A

```
// Single-phase linear load, 800 kVA  
  
LINEARLOAD      Name = LinLoad1  
                 From = 4160_A  
                 kV = 4160                kVA = 800  
                 DF = 0.85  
                 kVAXfmr = 1000  
                 %R = 0.5                 %X = 6.0
```

Note: kV is xfmr high side rating.

SuperHarm Data Preparation - cont

SuperHarm Device: **NONLINEARLOAD**

- Example: 480 V, 250 kVA, dc Drive (3-phase rating)

```
// Single-phase nonlinear load, 250 kVA

NONLINEARLOAD      Name = ASD1
                   Bus = 480BUS
                   kV = 0.277      kVA = 83.0      DF = 0.75
                   TABLE = {
                       { 1,      100.0,   -75.0},
                       { 5,      33.6,    156.0},
                       { 7,      1.6,   -151.0},
                       {11,      8.7,   -131.0},
                       {13,      1.2,    54.0},
                       etc.
                   }
```

SuperHarm Data Preparation - cont

SuperHarm Device: **SERIESFILTER**

- Example: 480 V, 450 kVAr 4.7th filter bank
@ bus 4801_A

```
// Single-phase filter bank  
  
SERIESFILTER          Name = Filter1  
                      CapBus = 4801_A      MidBus = Fil1_A  
                      IndBus = Ground  
                      kV = 0.277           kVA = 150  
                      Harmonic = 4.7
```

SuperHarm Data Preparation - cont

SuperHarm Device: TRANSFORMER

- Example: 1500 kVA, 13.8kV / 480 V
 transformer, $Z_{tx} = 6\%$

```
// Single-phase transformer  
  
TRANSFORMER    Name = StepTran            MVAB.HX = 0.500  
                 X.1 = 480BUS            X.2 = GROUND  
                 H.1 = SERVENT          H.2 = GROUND  
                 %X.HX = 6.0            KV.X = 0.277  
                 KV.H = 7.967
```

SuperHarm Data Preparation - cont

SuperHarm Device: **VSOURCE**

- Example: 18.8kV Source @ bus SRC1_A

```
// Single-phase voltage source  
  
VSOURCE      Name = UTILSRC  
              Bus = SRC1_A      Freq = 60.0  
              Mag = 7967        Ang = 0.0
```

SuperHarm Data Preparation - cont

Block and Line Comments:

- // Comment line (anywhere on line)
- ! Comment line (must be in column 1)
- /* - */ Block comment (everything in between)

SuperHarm Data Preparation - cont

#DEFINE and #UNDEF:

- #DEFINE Identifier Text_String

Example: #DEFINE 480LNV = 277.1281

Mag = 480LNV

- #UNDEF Identifier

SuperHarm Data Preparation - cont

DISCARD and RETAIN:

- DISCARD

Currents = Yes | No

CURRENTLIST = { Asd1, Drive1, Arc1 }

- RETAIN

Voltages = Yes | No

VOLTAGELIST = { Bus1, Bus2 }

SuperHarm Data Preparation - cont

#INCLUDE:

- #INCLUDE “FileSpec”

- #INCLUDE “FileSpec” (Param_1, Param_2,...)

%n - replacement parameters

SuperHarm Data Preparation - cont

Inline Math:

- ❑ Mathematical expression: @”expression”
- ❑ RPN Notation

Example:

$$\frac{480}{\sqrt{3}} = 480 \ 3 \ \text{SQRT} \ /$$

SuperHarm Data Preparation - cont

SCAN:


- ❑ SCAN directive applies one or more constant current sources to the system

```
// Frequency Scan Request  
  
SCAN          Name = Scan1  
              Bus = 480_A   Ang = 0  
              FMin = 60.0   FInc = 10       FMax = 1500
```


Converter Harmonic Characteristics

- ❑ Characteristic harmonics for different types of drives are different.
- ❑ Contents of the harmonic spectrum change with the operation condition.
- ❑ For a continuous current mode operation, to predict the harmonic generated by the drive - assume the ac line current with square wave waveshape can generate acceptable results.
- ❑ Even with a balanced ac supply, the operation of a semiconverter can generate even harmonics.




Three-Phase Semiconverter

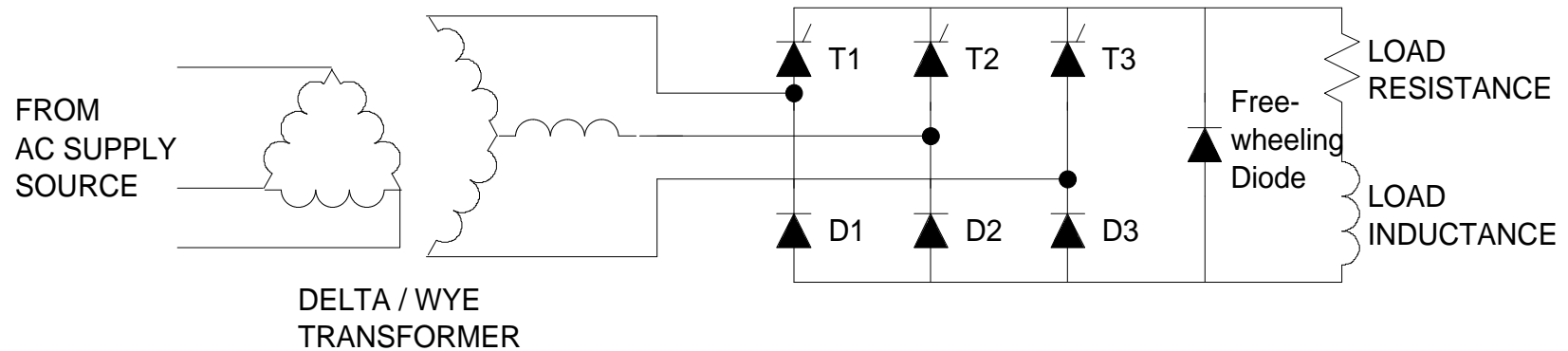

Three-Phase Semiconverter - cont

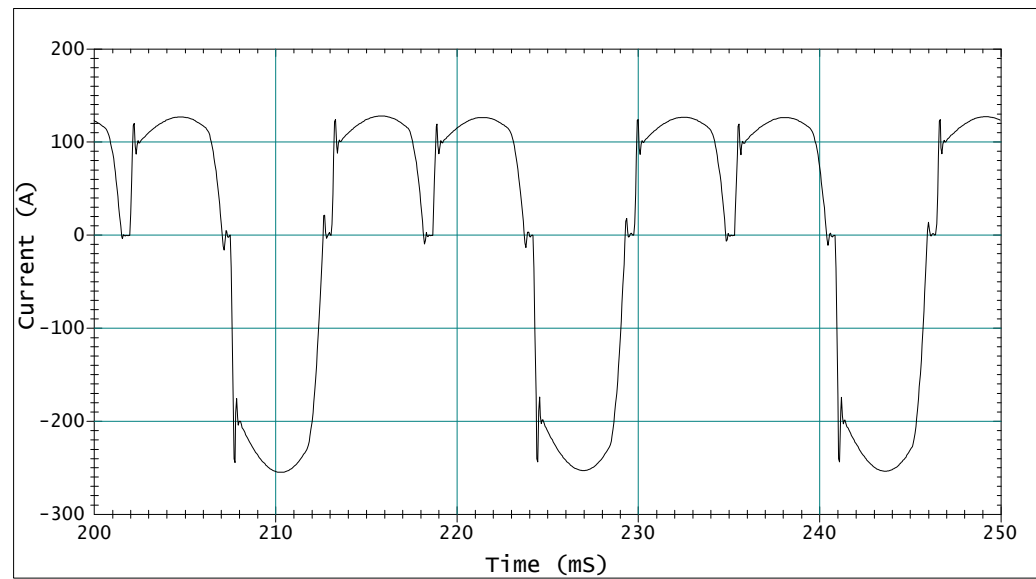

Three-Phase Semiconverter - cont

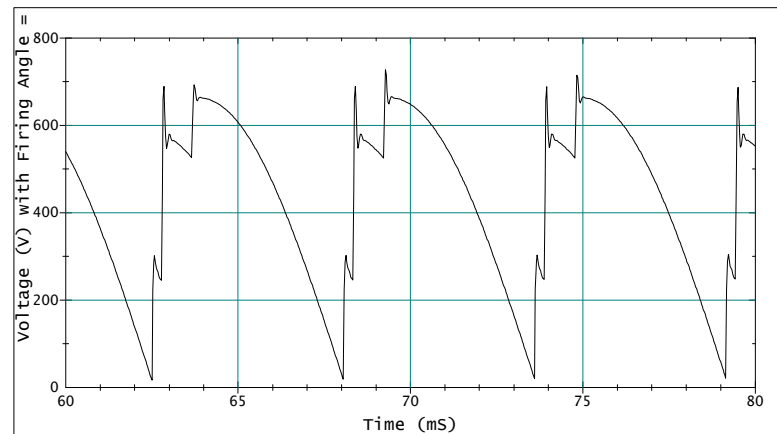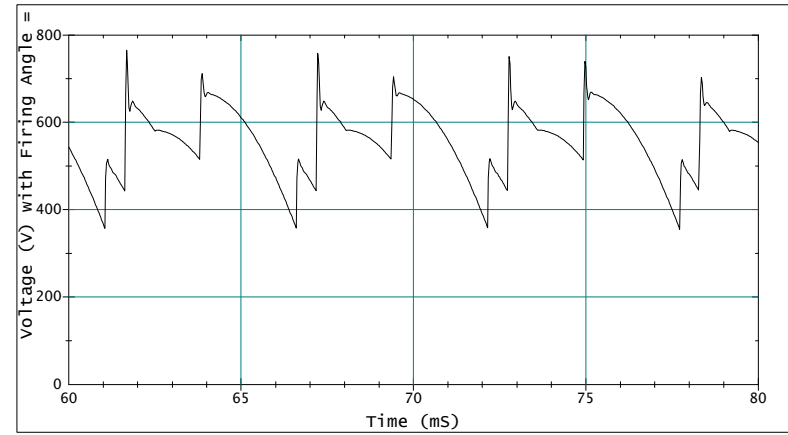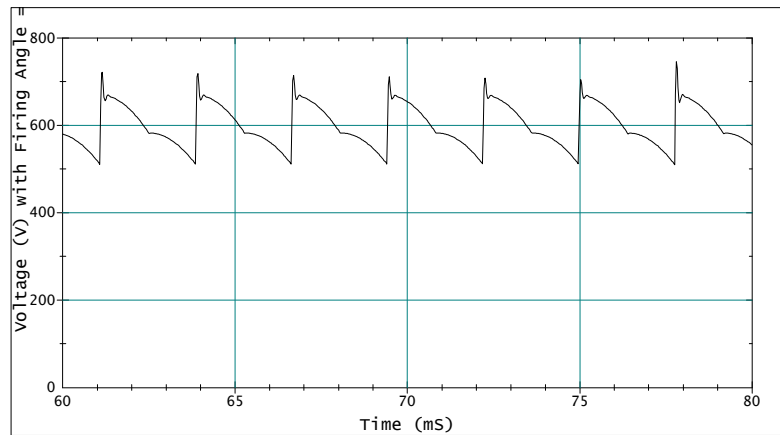

Three-Phase Semiconverter - cont



Three-Phase Semiconverter - cont

$$a_{n=2m} = \frac{2I_{dc}}{np} \sin\left(n\frac{p}{6}\right)(1 - \cos na)$$

for $n=2m, m=1, 2, 3, \dots$

$$b_{n=2m} = \frac{-2I_{dc}}{np} \sin\left(n\frac{p}{6}\right) \sin(na)$$

$$a_{n=2m+1} = \frac{-2I_{dc}}{np} \cos\left(n\frac{p}{6}\right) \sin(na)$$


for $n=2m+1, m=0, 1, 2, 3, \dots$

$$b_{n=2m+1} = \frac{2I_{dc}}{np} \cos\left(n\frac{p}{6}\right) [1 + \cos(na)]$$

Three-Phase Semiconverter - cont


$$|C_{n=2m}| = \sqrt{a_n^2 + b_n^2}$$
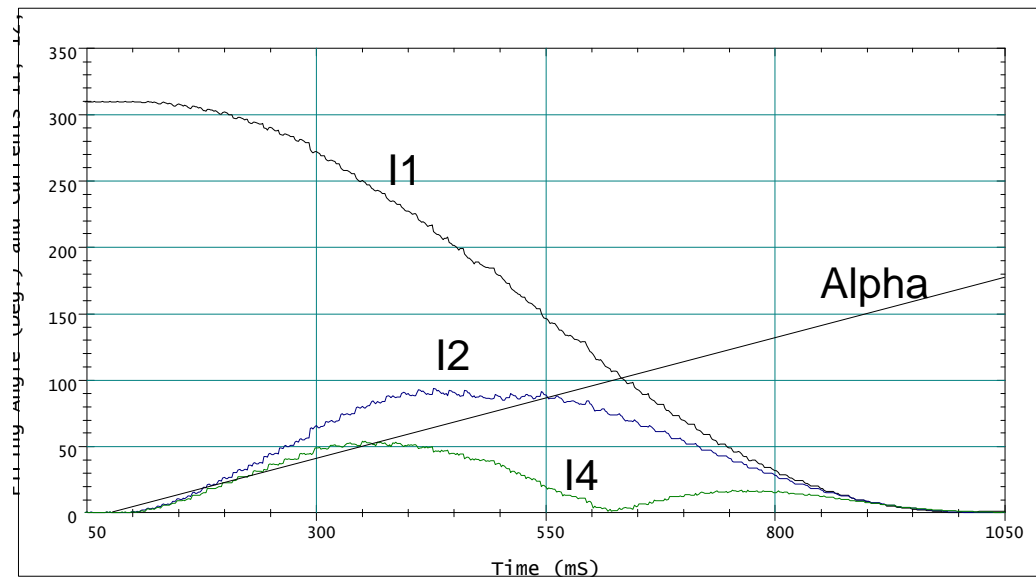
$$= \frac{2\sqrt{2}I_{dc}}{np} \sin\left(n\frac{p}{6}\right) \sqrt{1 - \cos(na)} \quad m=1, 2, 3, \dots$$



Fundamental and Even Harmonics

Three-Phase Semiconverter - cont

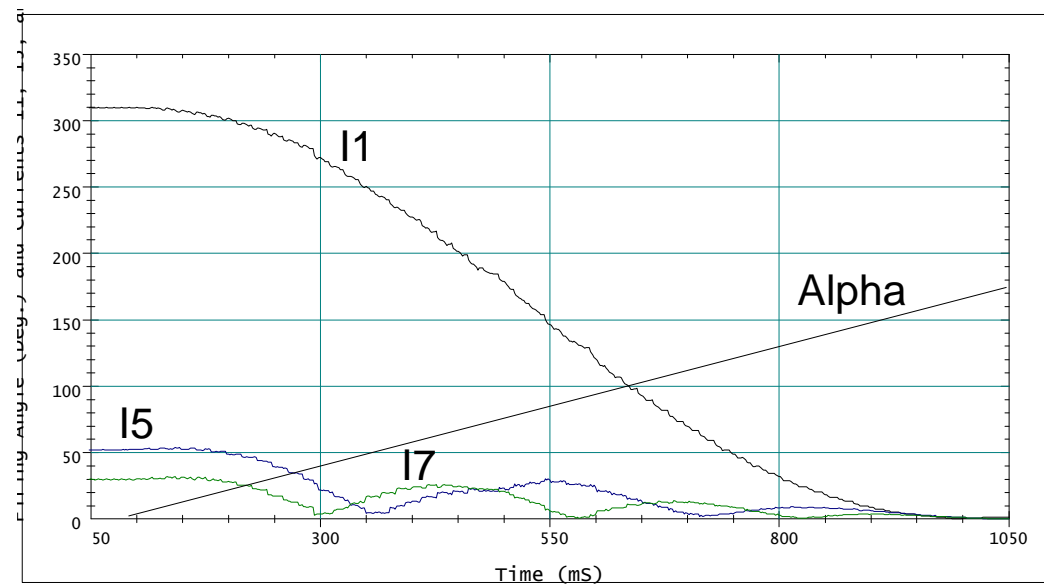


Fundamental and Odd Harmonics

Three-Phase Full-Converter

Average DC output voltage
for three-phase full converter
under idealized condition.

$$\begin{aligned}V_{dc} &= \frac{3\sqrt{3}V_{lg-peak}}{p} \text{Cosa} \\ &= \frac{3\sqrt{2}V_{ll-rms}}{p} \text{Cosa} \\ &= 1.35V_{ll-rms} \text{Cosa}\end{aligned}$$

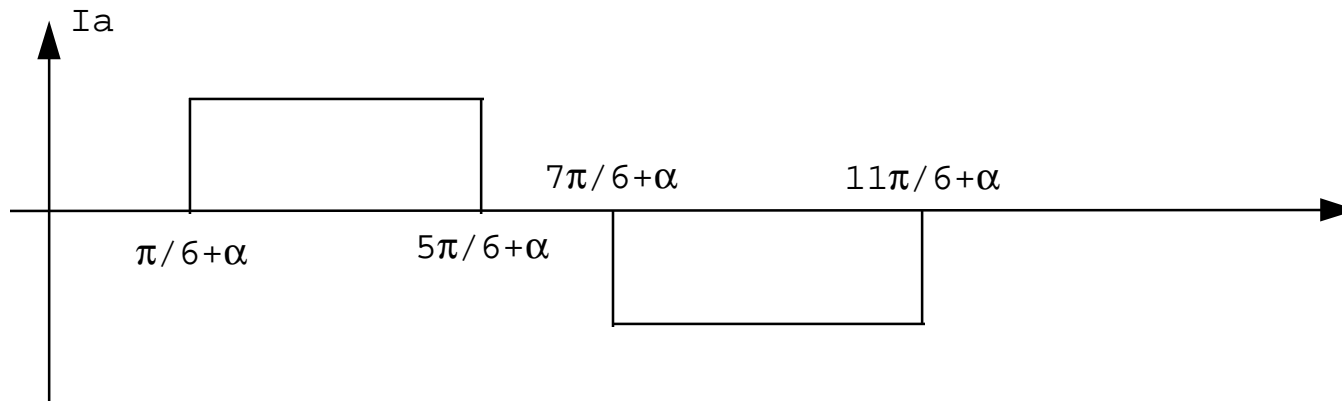Idealized line current waveform for three-phase
full converter.



Three-Phase Full-Converter - cont

Characteristic current harmonics for three-phase full converter under idealized condition

$$i_a(t) = \sum_{n=1,3,5,\dots}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$a_n = \frac{1}{p} \int_0^{2p} i_a(t) \cos n\omega t d(\omega t) \qquad b_n = \frac{1}{p} \int_0^{2p} i_a(t) \sin n\omega t d(\omega t)$$


$$= -\frac{4I_a}{np} \sin \frac{np}{3} \sin na \qquad = \frac{4I_a}{np} \sin \frac{np}{3} \cos na$$

or



$$i_a(t) = \sum_{n=1,3,5,\dots}^{\infty} \sqrt{2} I_n \sin(n\omega t + \mathbf{f}_n)$$

$$I_n = \frac{\sqrt{(a_n^2 + b_n^2)}}{\sqrt{2}} = \frac{2\sqrt{2}I_a}{np} \sin \frac{np}{3} \qquad \mathbf{f}_n = \tan^{-1} \frac{a_n}{b_n} = -na$$

ASD Types - dc Motor Drive

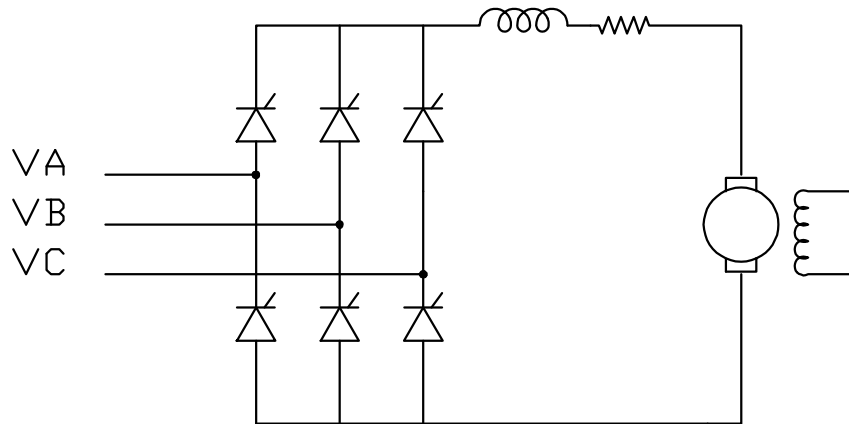




Motor Voltage & Current

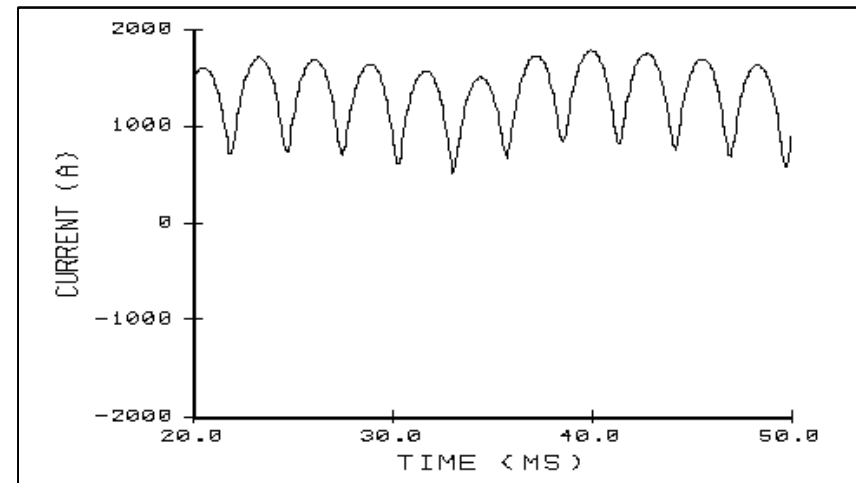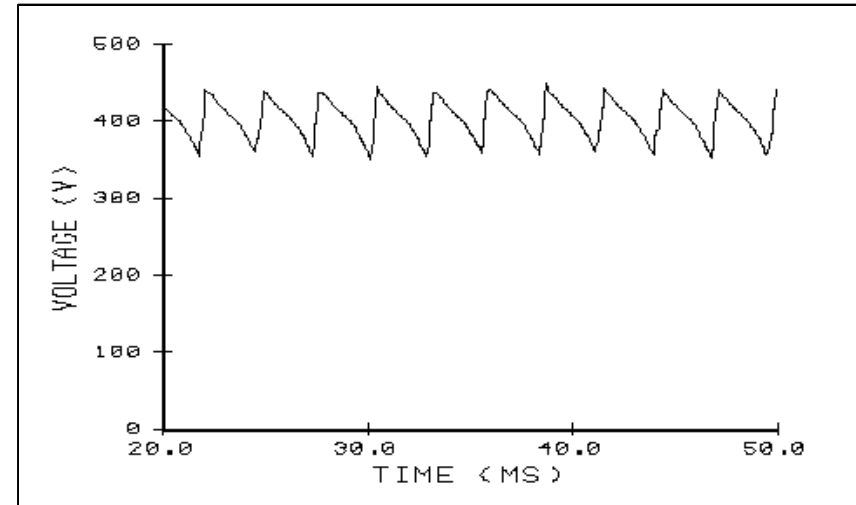


Characteristics and Applications:

- ❑ dc drives provide excellent control of both speed and torque
- ❑ Sizes range into 1000's of HP
- ❑ dc motor drive systems can have significant reactive power requirements.

dc Motor Drive - Snapshot #1

  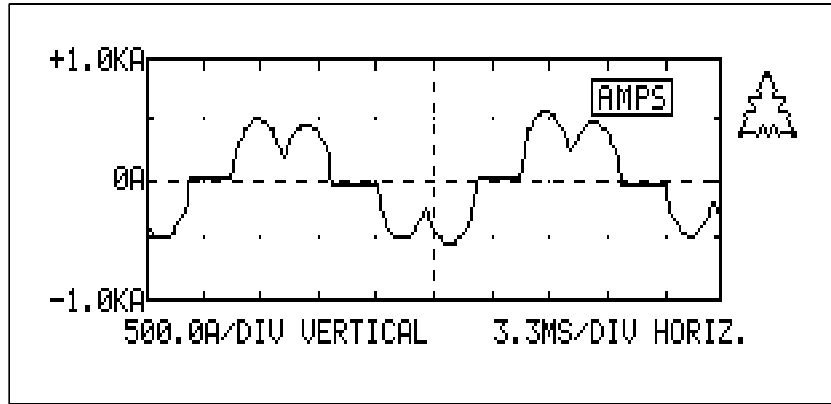


ASD Types - Current Source Inverter

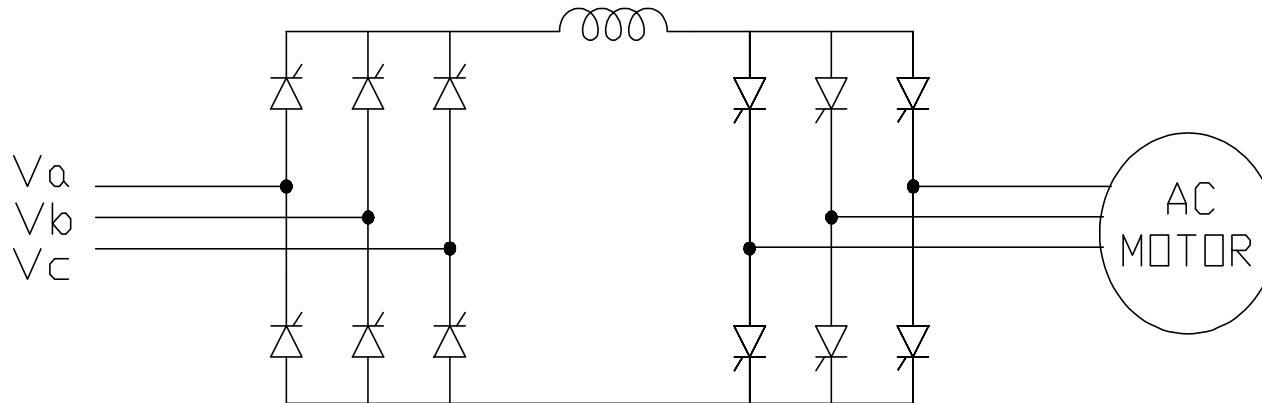


Characteristics and Applications:

- ❑ dc inductance maintains constant dc current for inverter
- ❑ CSI drives used for very large motors and high-inertia loads
- ❑ Power factor may be poor due to phase control of rectifier

Motor Voltage & Current

 


ASD Types - Voltage Source Inverter

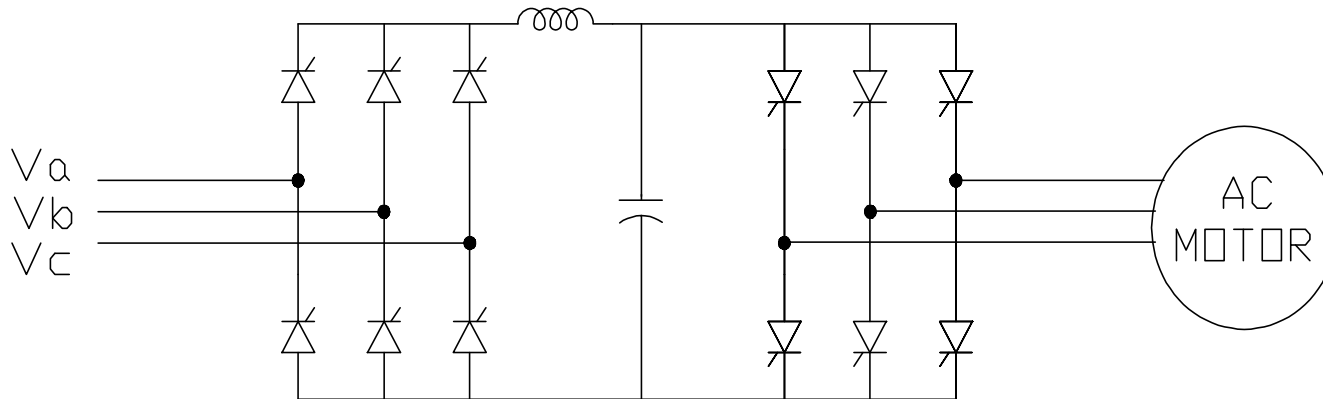


Characteristics and Applications:

- ❑ simple design, can handle multiple motors
- ❑ input (true) power factor can be poor due to high harmonic distortion of input currents
- ❑ is now being replaced in popularity by PWM type

Motor Voltage & Current

 


ASD Types - PWM Inverter

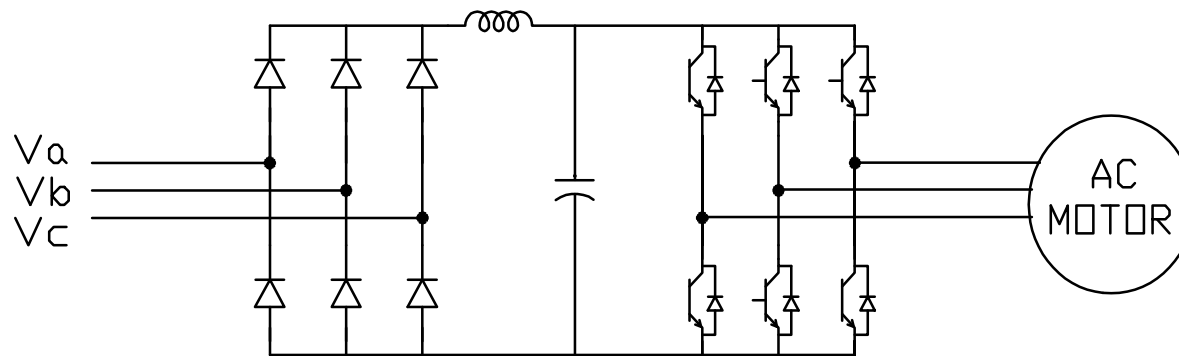

Characteristics and Applications:




- ❑ used in all types of applications (e.g. HVAC) for motors < 500 Hp
- ❑ rectifier operates uncontrolled
- ❑ input currents can have high harmonic distortion, causing poor (true) power factor
- ❑ may be very sensitive to transient voltages on ac system

Motor Voltage & Current

 



PWM Drive - Snapshot #1

PWM ASD with small (or no) input choke:


 
 
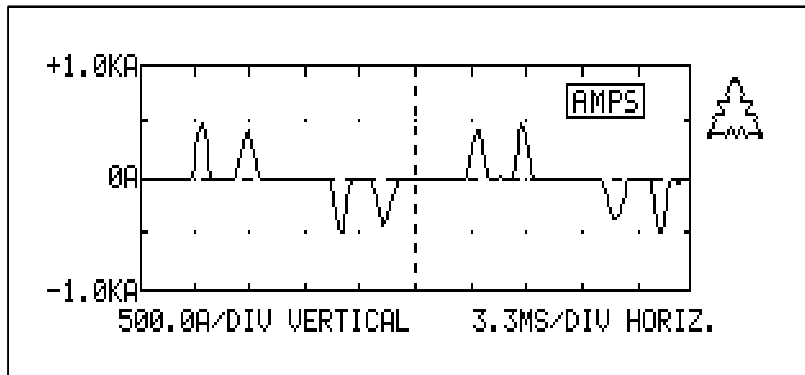


PWM Drive - Snapshot #2

 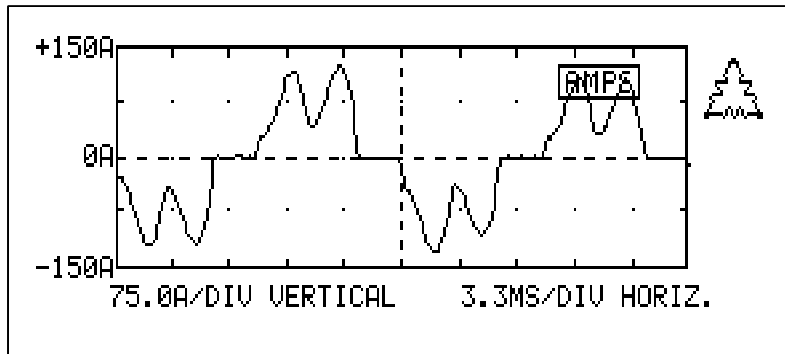PWM ASD with approximately 3% input choke:



Harmonic Distortion - Definition

 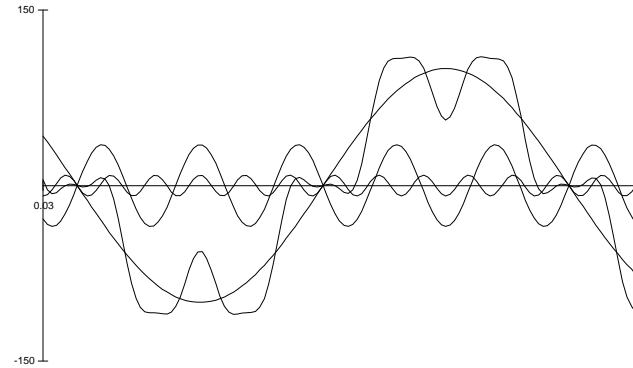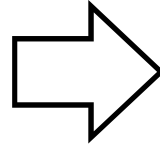 

Standards for Harmonics

IEEE 519-1992:

- ▶ Harmonic current injection limits for individual customers
- ▶ Harmonic voltage distortion limits for the overall system

IEC 555-2:

- ▶ Harmonic current injection limits for individual loads under 16 amps

ANSI/IEEE C57.110-1991:

- ▶ Transformer derating requirements

IEEE 519-1992 - What Does it Mean?

Harmonic Current Limits - Customer Responsibility

Isc/I(load)	<11	11<h<17	17<h<23	23<h<35	35<h	TDD
<20	4.0	2.0	1.5	0.6	0.3	5.0
20 - 50	7.0	3.5	2.5	1.0	0.5	8.0
50 - 100	10.0	4.5	4.0	1.5	0.7	12.0
100 - 1000	12.0	5.5	5.0	2.0	1.0	15.0
>1000	15.0	7.0	6.0	2.5	1.4	20.0

Values shown are in percent of rated load current

SCR = short circuit ration (utility short circuit current at point of common coupling divided by customer "rated" load current)

Harmonic Voltage Limits - Utility Responsibility

Bus Voltage	Maximum Individual Harmonic Component (%)	Maximum THD (%)
Below 69 kV	3.0%	5.0%
69 kV to 138 kV	1.5%	2.5%
Above 138 kV	1.0%	1.5%

Standards for Harmonics - cont

IEC 555-2:

Lighting Equipment (Table C)

Harmonic Order	Maximum Percent
2	2%
3	30% (PF)
5	10%
7	7%
9	5%
11-39	3%

Power Supplies (Table D)

	Relative (mA/W)	Absolute (A)
Odd Harmonics		
3	3.6	1.08
5	2	0.6
7	1.5	0.45
9	1	0.3
11-39	$0.6 \times (11/n)$	$0.18 \times (11/n)$
Even Harmonics		
2	1	0.3
4	0.5	0.15

Standards for Harmonics - cont

Transformer Derating Requirements:

- ▶ ANSI/IEEE Standard C57.110-1991
 - ▶ Derating method that starts with a given load current spectrum and then determines the amount of this current that would cause the same losses as a purely sinusoidal current.


- ▶ K - Factor
 - ▶ Ability of a transformer to withstand increased eddy current losses due to harmonic load current.

Sources of Harmonics


- ❑ Saturable devices - transformers and nonlinear reactors
- ❑ Arcing devices - arc furnaces, welders and fluorescent lighting
- ❑ Power electronics equipment - adjustable speed motor drives, dc motor drives and electronic power supplies

- ▶ Notching of the input voltage waves is a normal characteristic of the switching that occurs in the power electronics of a rectifier during continuous current operation.

Voltage Notching Snapshot

 


Expanded Waveform

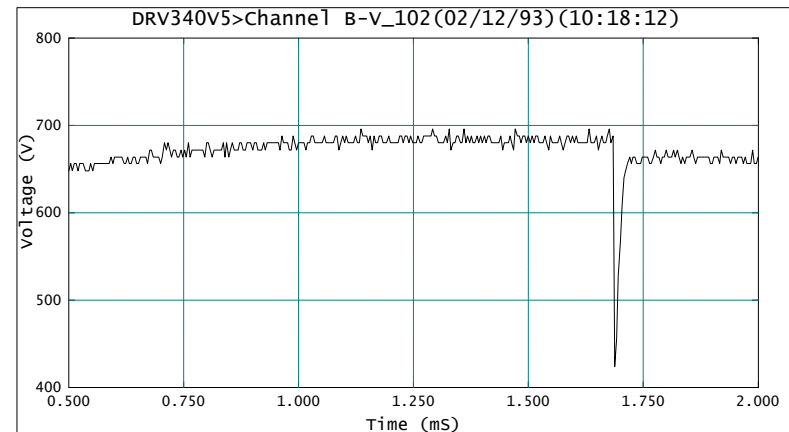

Harmonics from Different Sources


- ▶ Low-order (3,5,7) harmonic currents from multiple similar sources add nearly arithmetically.
- ▶ Higher-order harmonic currents will tend to cancel each other.
- ▶ Delta-wye transformer connections can have a significant influence on harmonic currents at the service entrance (especially 3rd).

Harmonic Cancellation - Office Building

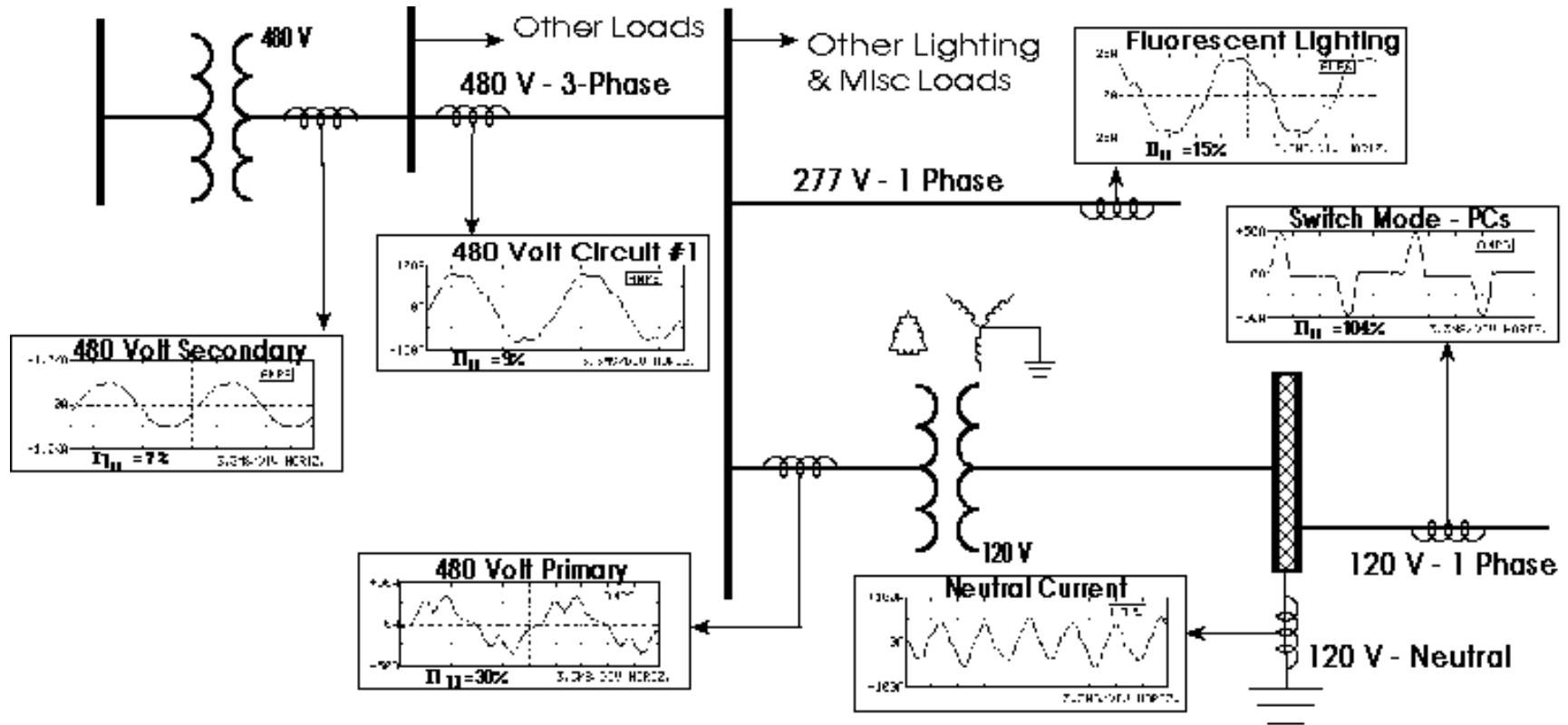


Representation of Nonlinear Loads

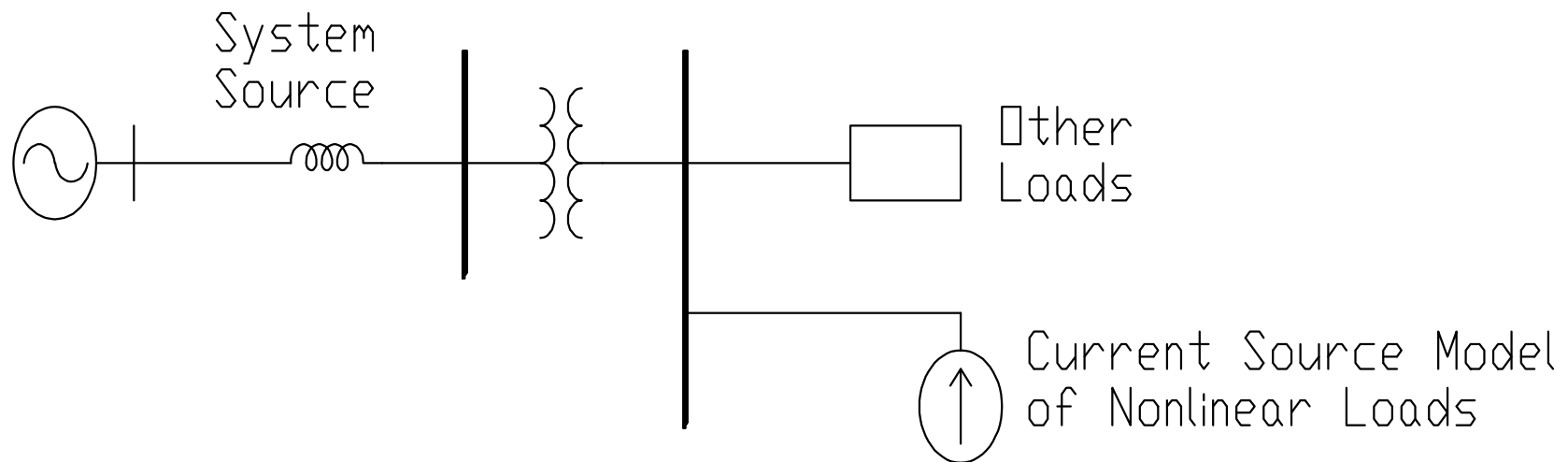In general, a nonlinear load can be represented as a source of harmonic currents:



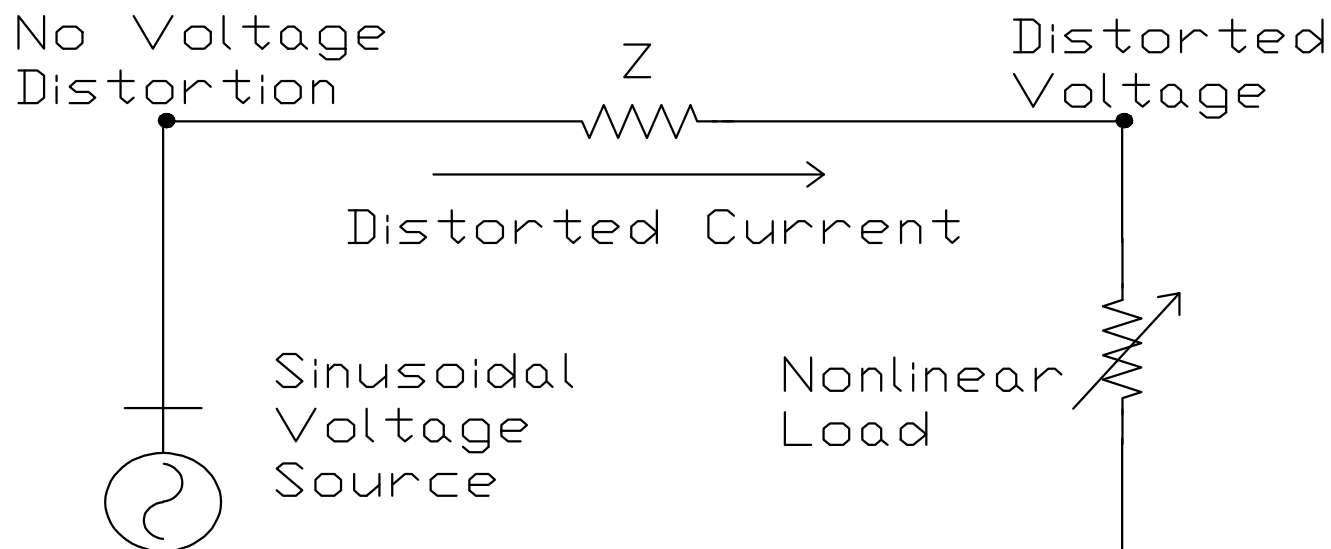- ❑ Nonlinear loads inject harmonic current components onto the system.
- ❑ The system impedance vs. frequency characteristics determine the harmonic voltage distortion levels.



System Response Characteristics

- Voltage distortion is a result of the voltage drop created across the equivalent power system impedance.
- At 60 Hz, power systems are primarily inductive. The equivalent inductance can be calculated:

$$L_{eq} = \frac{X_{sc}}{2\pi * f}$$

X_{sc} = system short circuit reactance

f = power system fundamental frequency (60 Hz)

Local Impedance Calculation

- At utilization voltages, the equivalent system reactance is usually dominated by local impedances (the stepdown transformer).
- In general: $X_{sc} \approx X_{\text{transformer}}$

$$X_t = \frac{(\text{kV}_{LV}^2) * Z_{pu}}{\text{MVA}} \Omega$$


Impedance vs. Frequency

At harmonic frequencies, the impedance of the equivalent inductance is:

$$X_h = 2 \cdot p \cdot f_h \cdot L_{eq} = 2 \cdot p \cdot 60 \cdot h \cdot L_{eq}$$

h = harmonic number

f_h = harmonic frequency

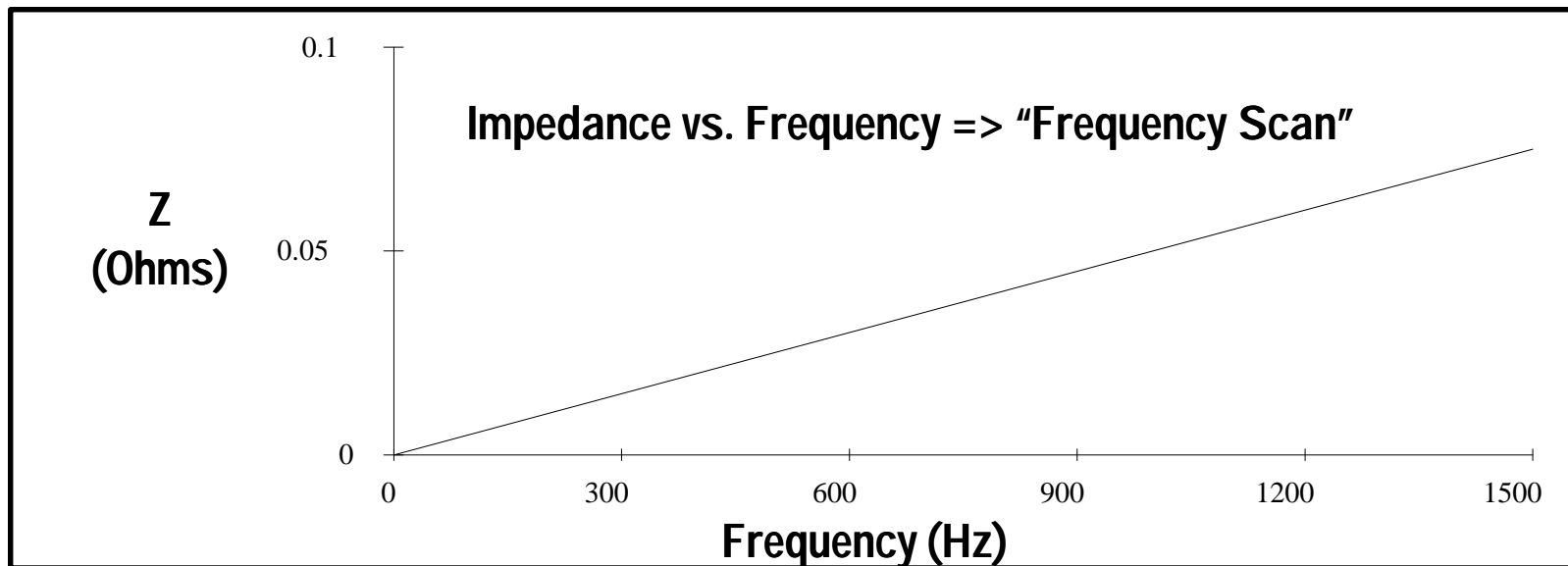

Voltage Distortion Calculation

$$V_{\text{THD}} = \sqrt{\frac{\sum V_h^2}{V_1^2}}$$

500 HP Drive, 1500 kVA, 6% Transformer

Harmonic Number h	Harmonic Current (Amps) I _h	System Impedance (Ohms) X _h	Harmonic Voltage (Volts) V _h
5	186	0.046	8.55
7	38	0.064	2.43
11	61	0.101	6.16
13	28	0.119	3.33


4.09%

$$V_{\text{THD}} = \sqrt{\frac{(8.55^2 + 2.43^2 + 6.16^2 + 3.33^2)}{\left(\frac{480}{\sqrt{3}}\right)^2}} = 4.09\%$$

Note: No capacitors installed

Effect of Shunt Capacitors

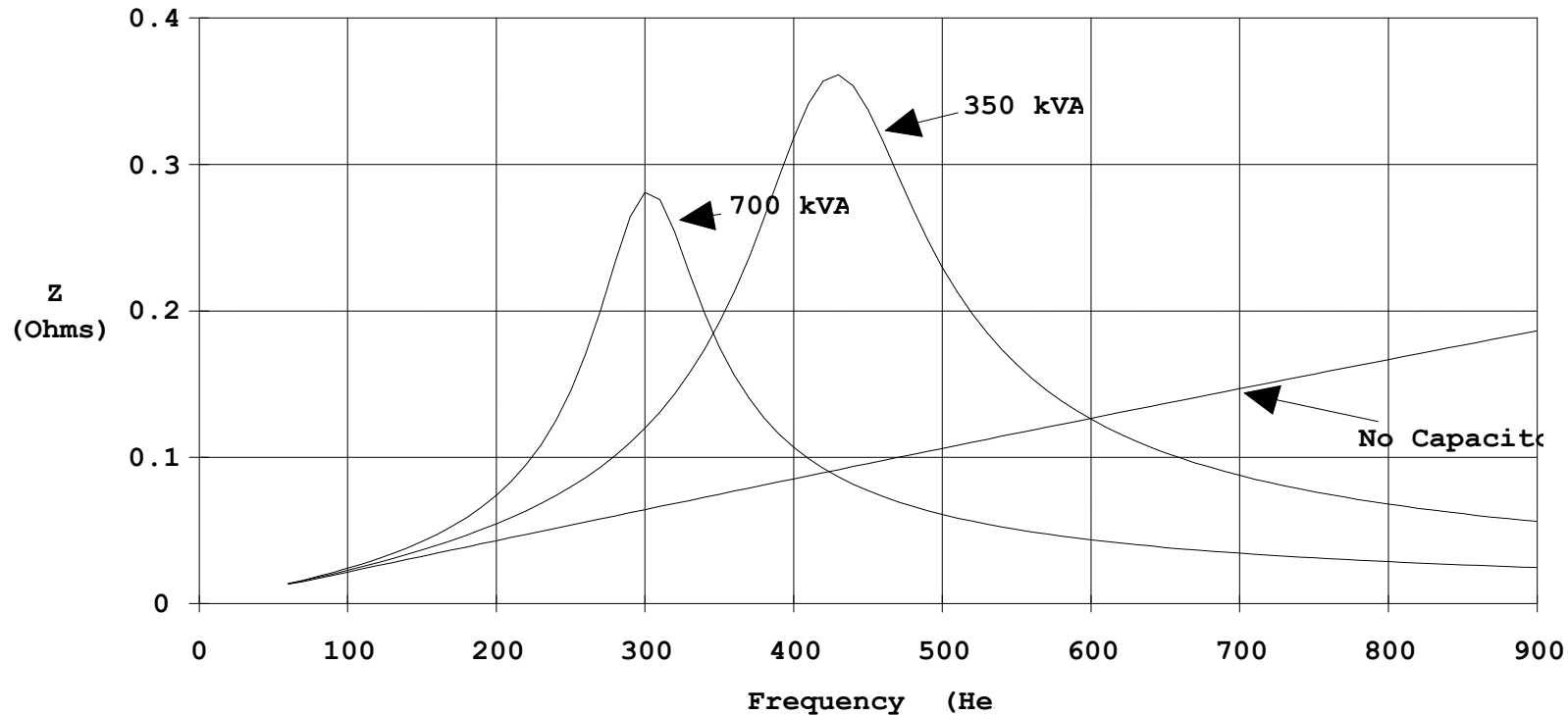- Shunt capacitors can dramatically alter the system frequency response. They create a parallel resonance that can magnify harmonic currents and cause increased voltage distortion levels.




Resonant Frequency

- At the frequency where the capacitive reactance (X_C) and the inductive reactance (X_L) are equal, the impedance seen by the nonlinear load becomes very large.
- This is known as the parallel resonant frequency and can be calculated from:

$$f_r = \frac{1}{2 \cdot p \cdot \sqrt{L \cdot C}} = \sqrt{\frac{MVA_{SC}}{MVA r_C}} \cdot 60$$

- If the **calculated frequency** corresponds to one of the **characteristic harmonic frequencies** of a nonlinear load, **high distortion** might be expected.


Location for Power Factor Correction

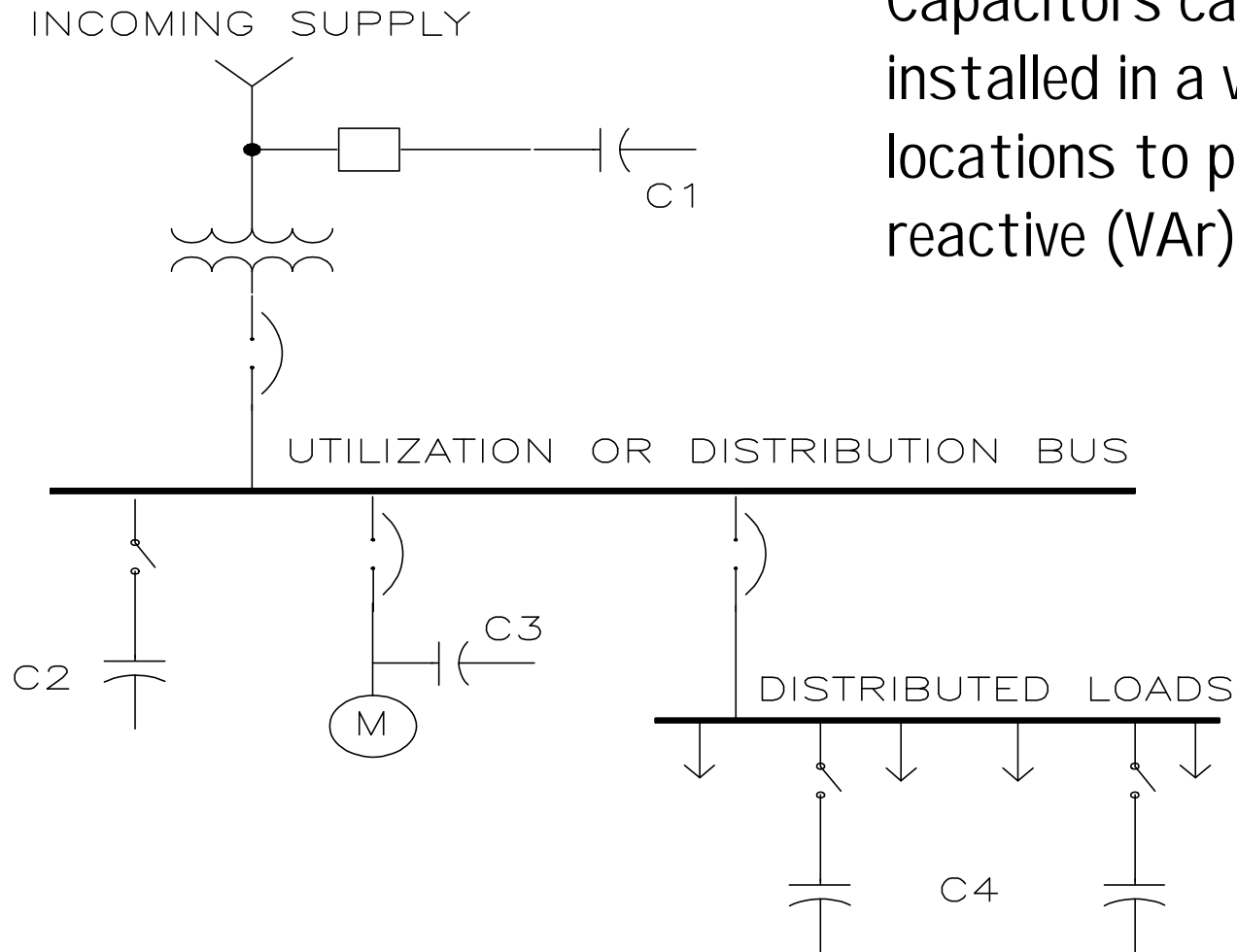

Capacitors can be installed in a variety of locations to provide reactive (VAR) power.

Displacement Power Factor Triangle

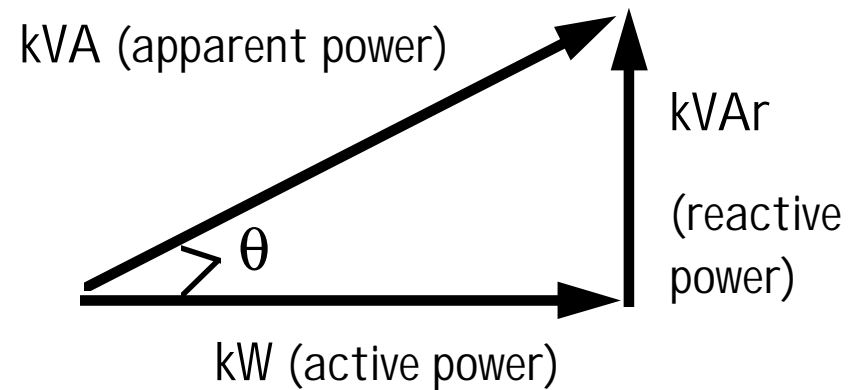- ▶ Displacement Power Factor is only equal to the true power factor if the voltage and current waveforms contain zero harmonic distortion.



$$\text{DPF} = \text{Cos}\theta = \frac{\text{kW}}{\text{kVA}}$$

$$\text{kVA} = \sqrt{(\text{kW}^2 + \text{kVAr}^2)}$$

Typical Power Factor of Loads


	<u>Displacement Power Factor</u>
Induction Motors	70-80
Diode Rectifiers (small ASDs)	95-98
Fluorescent Lighting	
Standard Ballast (also HID)	70
Electronic Ballast	90
Phase Controlled Rectifier (DC Drives) (Large ASDs)	40-90
Arc Furnaces	75-90
Arc Welding	35-60
Resistance Welding	40-60

True Power Factor - Definition

- ❑ Capacitors can only fully correct displacement power factor (only provide kVAr at fundamental frequency.)
- ❑ When harmonic currents or voltages are present, volt-amperes at the higher harmonic frequencies will decrease the true power factor.

An example follows using the line current and voltage of a small ASD.

ASD Line Current

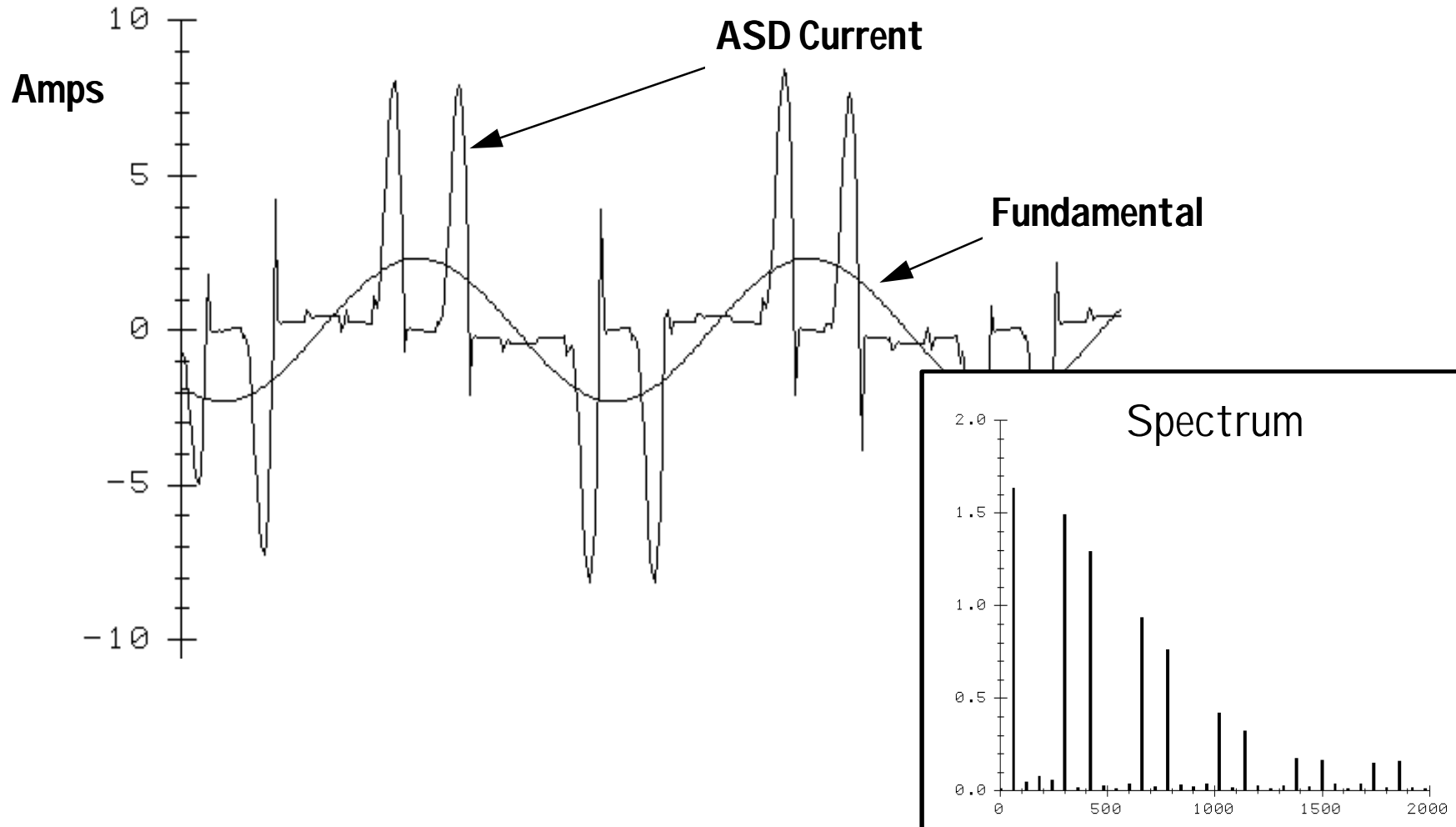

Calculations for ASD Line Current

- The rms value of the ASD Line current (from the provided spectrum) is:

$$I_{\text{rms}} = \sqrt{\sum_{h=1}^{\infty} I_h^2} = \sqrt{(1.63^2 + 1.50^2 + \dots + 0.17^2)} = 2.91 \text{ amps}$$

- Similarly the Total Harmonic Distortion (THD) can be calculated using:

$$\text{THD} = \frac{\sqrt{I_2^2 + I_3^2 + I_4^2 + \dots}}{I_1} = \frac{2.414}{1.63} = 1.48 = 148\%$$

- And the Crest Factor (CF) is defined as:

$$\text{CF} = \frac{I_{\text{peak}}}{I_{\text{rms}}} = \frac{8.0}{2.913} = 2.746$$

True Power Factor Calculation

- For the ASD line current assume the fundamental component of the current is in phase with the voltage, therefore:

$$\theta = 0^\circ$$

- ▶ And the displacement power factor is equal to unity:

$$\text{DPF} = \cos \theta = 1.0 = 100\%$$

- ▶ The real power consumed (single phase, first order approximation) is:


$$P = V_1 \cdot I_1 \cdot \cos \theta = (480\text{V})(1.63\text{A})(1.0) = 782.4\text{W}$$

- ▶ Finally, the true power factor is:

$$\text{TPF} = \frac{P}{V_{\text{rms}} \cdot I_{\text{rms}}} = \frac{782.4\text{W}}{(480\text{V})(2.913\text{A})} = 0.56 = \underline{\underline{56\%}}$$


Harmonic Waveform and Spectrum

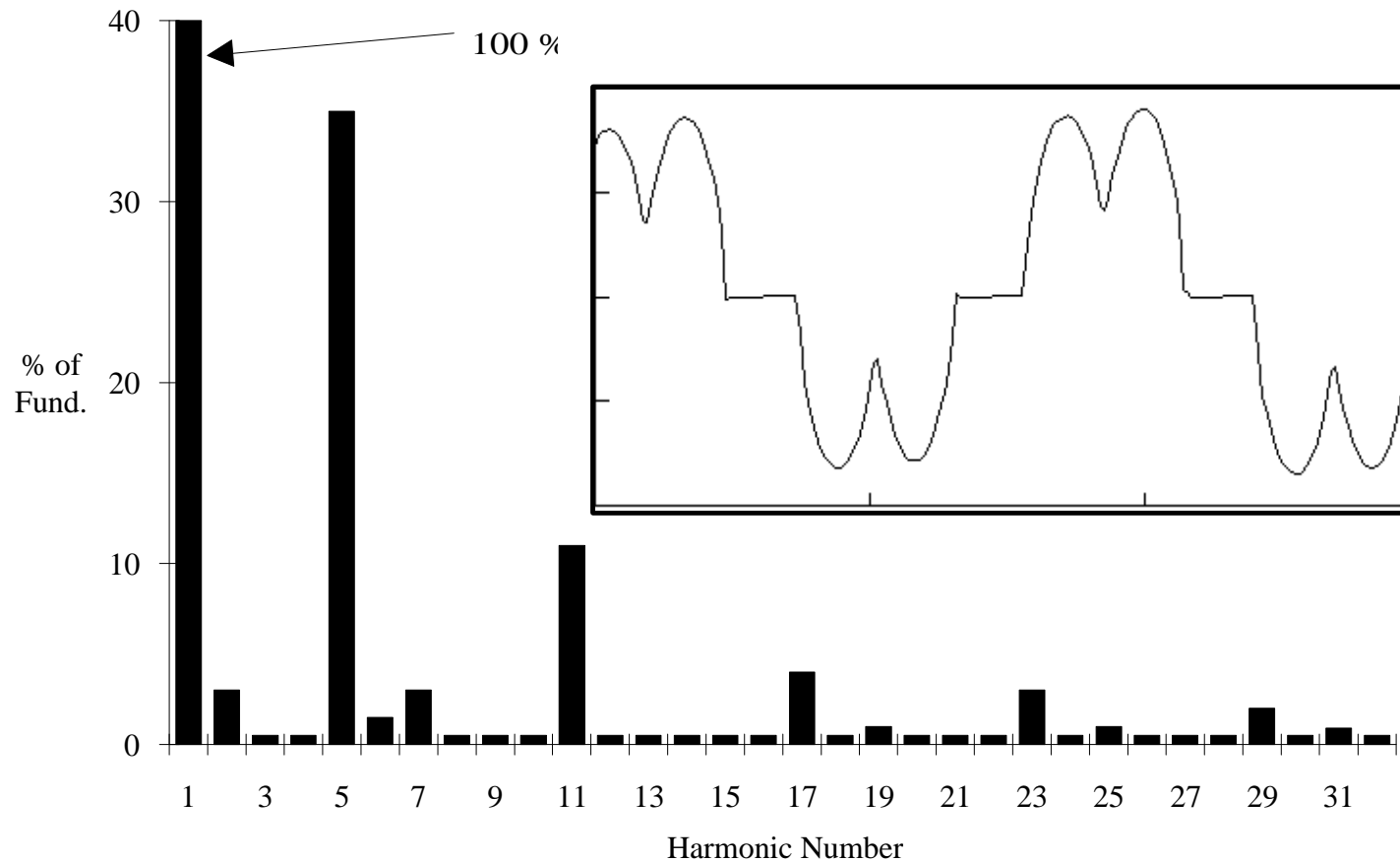Individual Frequencies and Magnitudes are Important!




Harmonic Reduction Methods

ASD Input Current Waveform

 


 **ASD Input Current Waveform
with 30° Phase Shift Through
Isolation Transformer**



Result is very good current distortion level, if approximately half of load is each waveform.

Impact of Transformer Connection

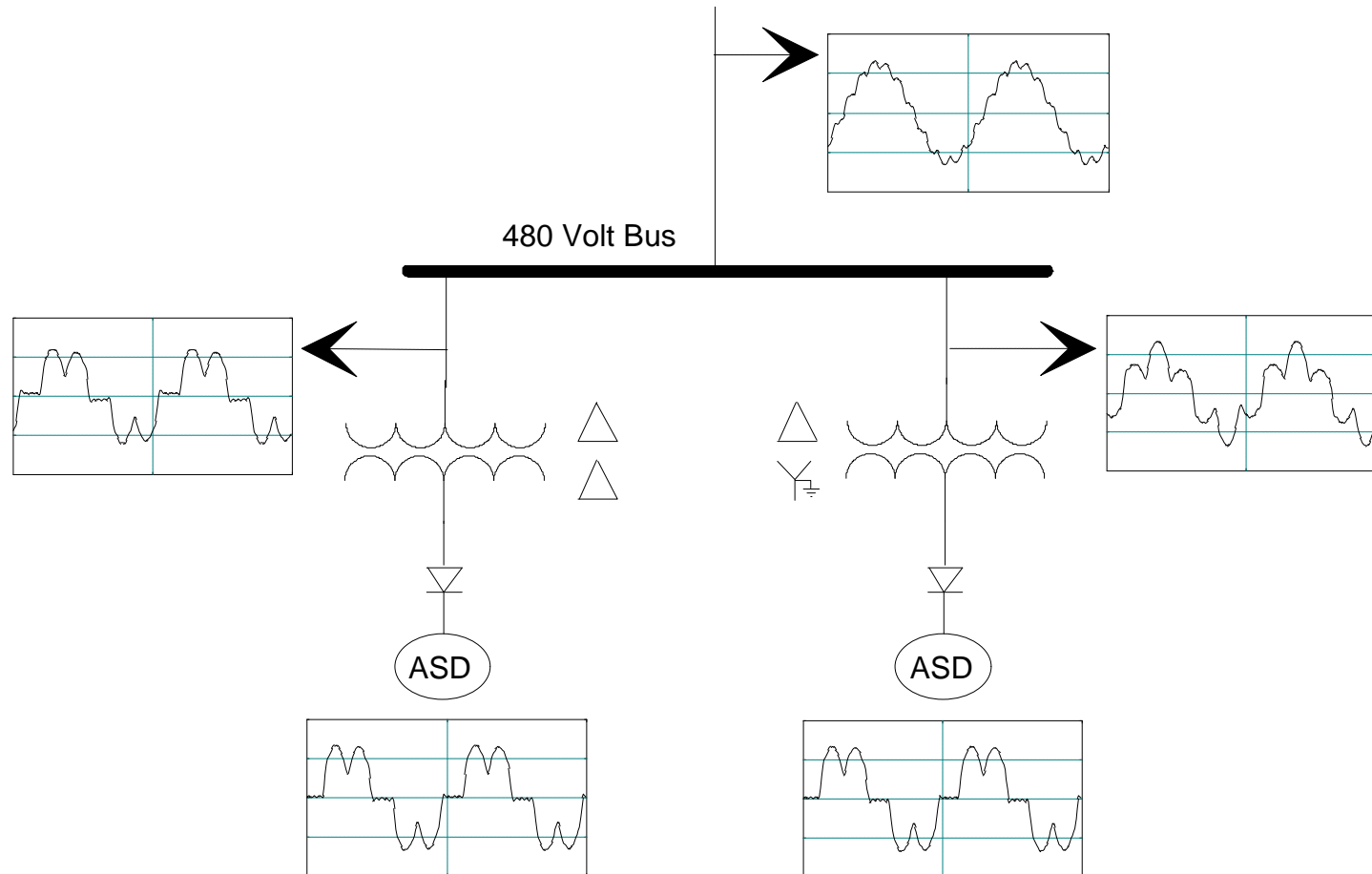


ISOXFMRS.SHA

Reduction Methods - Basic Filter Design

The general method for applying filters is as follows:

- ❑ Apply one single tuned filter first, and design it for the lowest generated frequency (i.e. 5th harmonic - 4.7th filter).
- ❑ Determine the voltage distortion at the low voltage bus, 5% is the commonly applied limit.
- ❑ Vary filter elements (tolerances) and check its effectiveness.
- ❑ Check the frequency response characteristic to verify that the newly created parallel resonance is not close to a harmonic frequency.
- ❑ If necessary, investigate the need for several filters, such as 5th and 7th.

Effect of Filter on Frequency Response

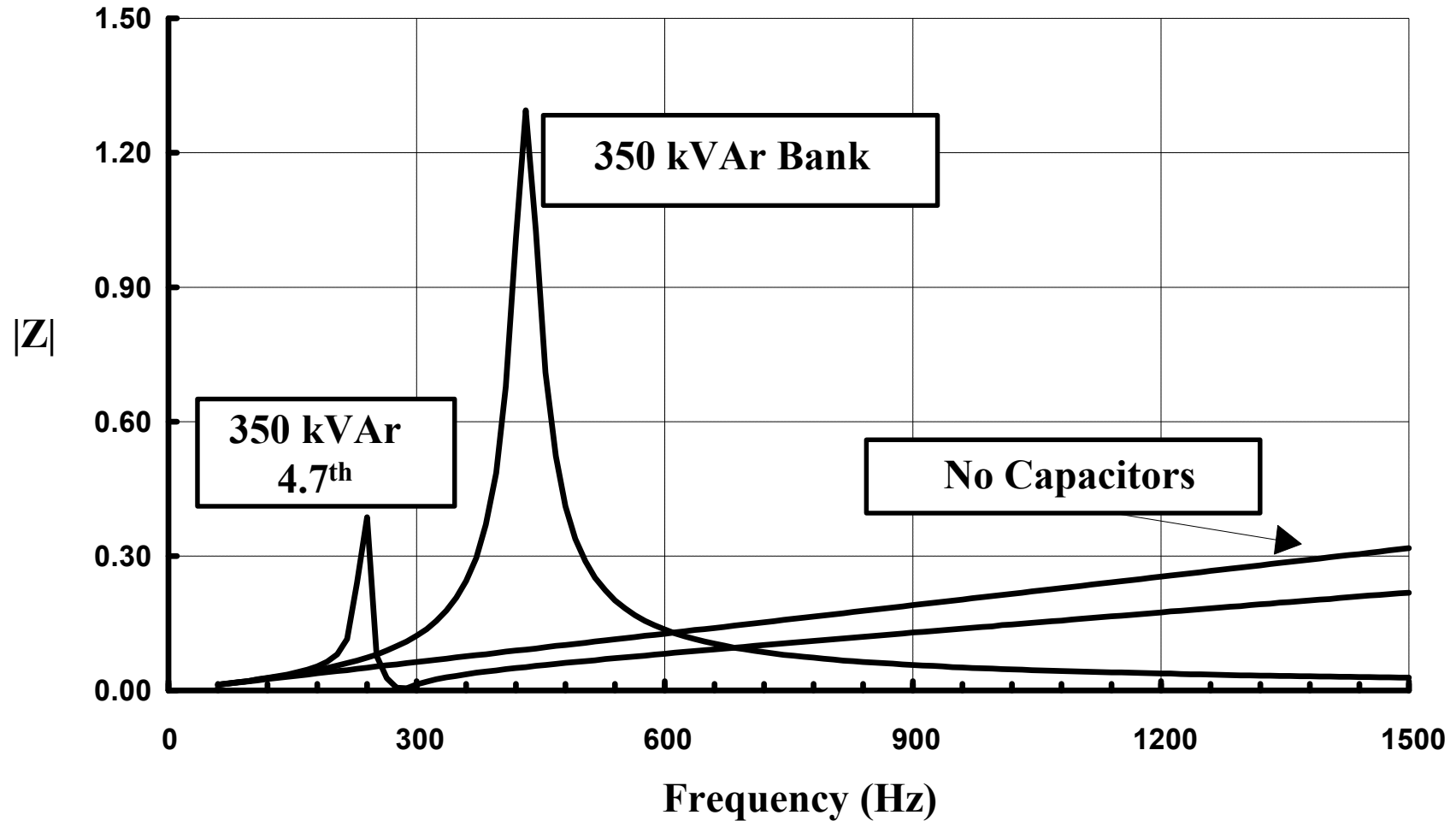

Example Filter Design Spreadsheet

Low Voltage Filter Calculations: Example Filter Specification			
SYSTEM INFORMATION:			
Filter Specification:	5 th	Power System Frequency:	60 Hz
Capacitor Bank Rating:	500 kVAR	Capacitor Rating:	480 Volts 60 Hz
Nominal Bus Voltage:	480 Volts	Derated Capacitor:	500 kVAR
Capacitor Rated Current:	601.4 Amps	Total Harmonic Load:	500 kVA
Filter Tuning Harmonic:	4.7 th	Filter Tuning Frequency:	282 Hz
Cap Impedance (wye):	0.4608 W	Cap Value (wye):	5756.5 uF
Reactor Impedance:	0.0209 W	Reactor Rating:	0.0553 mH
Filter Full Load Current:	629.9 Amps	Supplied Compensation:	524 kVAR
Transformer Nameplate: (Rating and Impedance)	1500 kVA 6.00%	Utility Side Vh: (Utility Harmonic Voltage Source)	1.00% THD
Load Harmonic Current:	30.00% Fund	Load Harmonic Current:	180.4 Amps
Utility Harmonic Current:	47.7 Amps	Max Total Harm. Current:	228.1 Amps
CAPACITOR DUTY CALCULATIONS:			
Filter RMS Current:	669.9 Amps	Fundamental Cap Voltage:	502.8 Volts
Harmonic Cap Voltage:	36.4 Volts	Maximum Peak Voltage:	539.2 Volts
RMS Capacitor Voltage:	504.1 Volts	Maximum Peak Current:	858.0 Amps

Important Parameters:


- Capacitor Size and Voltage
- Tuning Frequency
- Reactor Impedance
- Capacitor Limits
- Reactor Current Rating (60 Hz and Harmonic)

CAPACITOR LIMITS: (IEEE Std 18-1980)

	Limit		Actual
Peak Voltage:	120%	←→	112%
Current:	180%	←→	111%
KVAR:	135%	←→	117%
RMS Voltage:	110%	←→	105%

Harmonic Filter Design - Case Study

 - **Problem Statement:** A plastics manufacturer is experiencing equipment problems, including capacitor bank fuses blowing, and a capacitor can failure. The plant engineer believes that the problem may be related to harmonics. He measures the following bus voltage waveform:




Oneline for Harmonic Analysis


Circuit for harmonic analysis:

FILTER_1.SHA



200 MVA
Source 13.8 kV

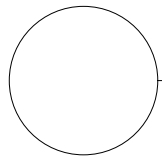

13.8kV/480V
1500 kVA
 $Z = 6.0\%$

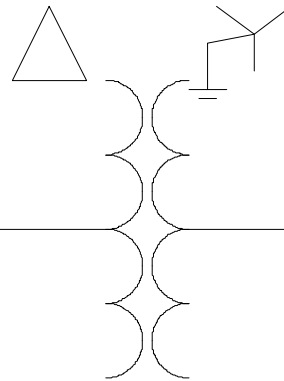

Drive Characteristic:

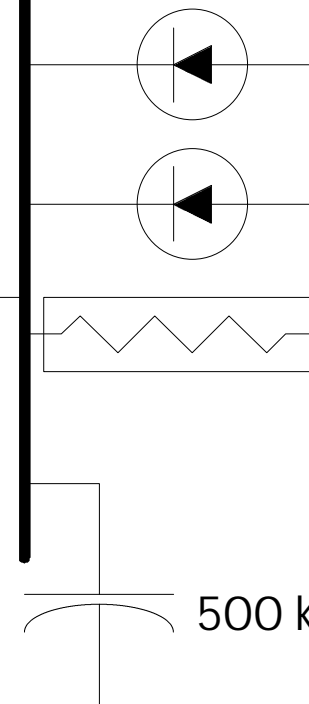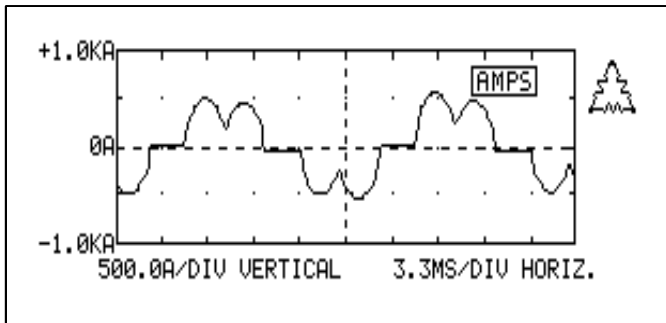

250 kVA ASDs
DF = 90%

500 kVA
Load
85 % PF

500 kVAr

SuperHarm Data Listing

Comment Section and Titles (TITLE)

```
//  
//      File Name:  FILTER_1.SHA  
//  
//      HarmFlo+ Case Study Workbook - Volume #2, Draft #1  
//  
//      Industrial case study.  Plant has one 480 Volt bus that  
//      feeds two 250 kVA ASDs and 500 kVA of additional motor  
//      and other miscellaneous loads.  Plant engineers are proposing  
//      to add 500 kVAr of power factor correction to increase power factor  
//      and to free up some transformer kVA.  
//  
//      This model is a single phase representation of the Utilty system  
//      and the plant.  All values are in single phase quantities.  
//  
TITLE          TITLE1 = "Industrial Filter Design Case Study"  
                TITLE2 = "HarmFlo+ Case Study Workbook - Volume 2"
```

SuperHarm Data Listing - cont

Source Equivalent (VSOURCE and BRANCH)

```
//  
//      Utility source, 200 MVA @ 13.8 kV  
//  
VSOURCE      NAME = UTILSRC  
              BUS = SRC      FREQ = 60.0  
              MAG = 7967     ANG = 0.0  
  
//  
//      Positive sequence source equivalent @ service entrance.  
//      All values in Ohms.  X to R ratio = 20  
//  
BRANCH       NAME = ZEQ  
              FROM = SRC      TO = SERVENT  
              R = 0.04761     X = 0.9522
```


SuperHarm Data Listing - cont

Transformer Model (TRANSFORMER)

```
//  
// Step down transformer @ service entrance.  
// 1500 kVA, 13.8 kV / 480 Volt, Z = 6 %  
//  
// The "@" symbol is used to do inline math. In this case  
// the Line to Ground voltage is calculated from the Line to Line  
// voltage.  
//  
  
TRANSFORMER      NAME = STEPTRAN MVAB.HX = 0.500  
                  X.1 = 480BUS      X.2 = GROUND  
                  H.1 = SERVENT     H.2 = GROUND  
                  %X.HX = 6.0      KV.X = @"0.480 3 SQRT /"  
                  KV.H = @"13.8 3 SQRT /"
```

SuperHarm Data Listing - cont

Miscellaneous Load Model (LINEARLOAD)

```
//  
//      Miscellaneous load on 480 Volt bus.  
//      Using the Linear Load model  
//      500 kVA of load. 166 kVA of single phase load.  
//  
  
LINEARLOAD      NAME = MISCLOAD  
                FROM = 480BUS      TO = GROUND  
                KV = 0.277          KVA = 166  
                DF = 0.85           %PARALLEL = 90.0  
                %SERIES = 10.0
```

ASD Characteristic

Adjustable-speed drive characteristic:

Total Drive rating: 500 Hp
Voltage: 480 V
Fundamental Current: 600 A

Harmonic	%	Amps
5	33.6	202
7	1.6	9.6
11	8.7	52.2
13	1.2	7.2

$$\text{THD} = \frac{\sqrt{I_2^2 + I_3^2 + I_4^2 + \dots}}{I_1} :$$

$$I_{\text{THD}} = 34.8\%$$

SuperHarm Data Listing - cont

ASD Models (NONLINEARLOAD)

```
//  
//      Model of the ASDs on the 480 Volt bus.  
//      2 - 250 kVA ASDs running full load & 75% pf  
//      Using the NonLinear Load model.  
//  
  
NONLINEARLOAD      NAME = ASD1  
                    BUS = 480BUS  
                    KV = 0.277      KVA = 83.0      DF = 0.75  
                    TABLE = {  
                        { 1,      100.0,      -75.0},  
                        { 5,      33.6,      156.0},  
                        { 7,      1.6,      -151.0},  
                        {11,      8.7,      -131.0},  
                        {13,      1.2,      54.0},  
                        {17,      4.5,      -57.0},  
                        {19,      1.3,      -226.0},  
                        {23,      2.7,      17.0},  
                        {25,      1.2,      -149.0}  
                    }
```

SuperHarm Data Listing - cont

Frequency Scan (SCAN)

```
//  
//      Frequency Scan Request (remove comment to activate)  
//  
//      SCAN      Name = Scan1  
//                BUS = 480BUS      ANG = 0  
//                FMIN = 60          FMAX = 1500      FINC = 10
```

Insert SCAN card in data file and SuperHarm will short all other sources and open all injected currents and perform a frequency scan at that bus.


Voltage Distortion - No Capacitors

h	I _h	X _h = h*X _t	V _h = I _h *X _h
5	202	0.046	9.29
7	9.6	0.064	0.62
11	52	0.101	5.25
13	7.2	0.119	0.86

$$V_{\text{THD}} = \sqrt{\frac{(9.29^2 + 0.62^2 + 5.25^2 + 0.86^2)}{277^2}} = 3.87\%$$

Effect of 500 kVAr Capacitor Bank

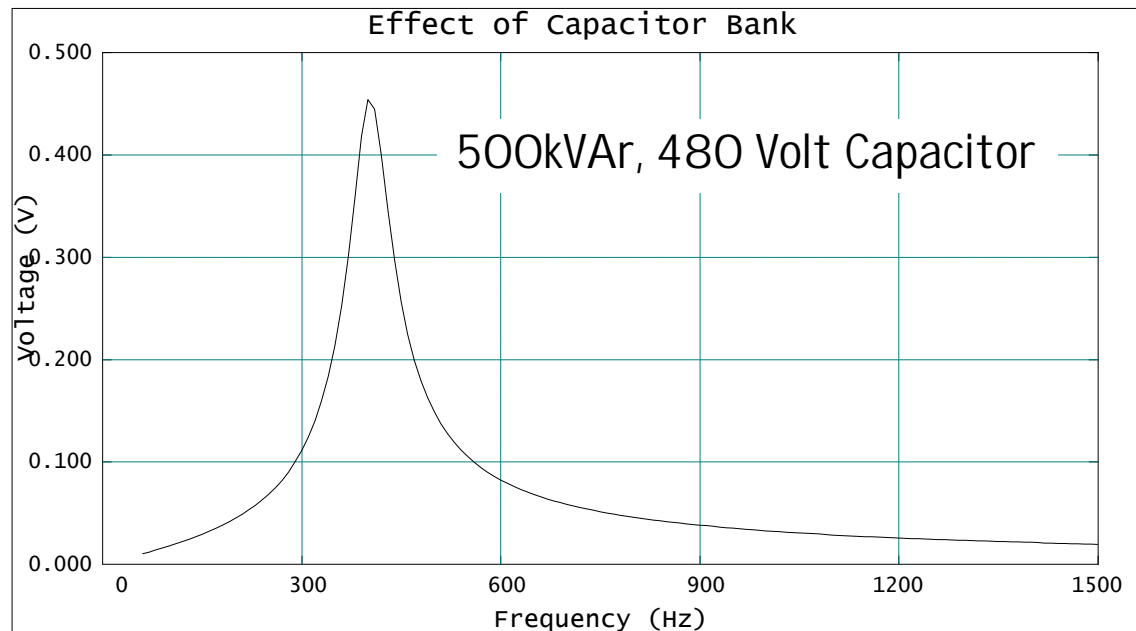
The 500 kVAr capacitor bank causes a resonance near the 7th harmonic, which can be calculated from the following equation and illustrated in the following plot. The distortion level increased to 8.29% with the addition of the bank.



Initial Solution?


would appear to be the application of a 7th harmonic filter.

The distortion increased to 19.6%!

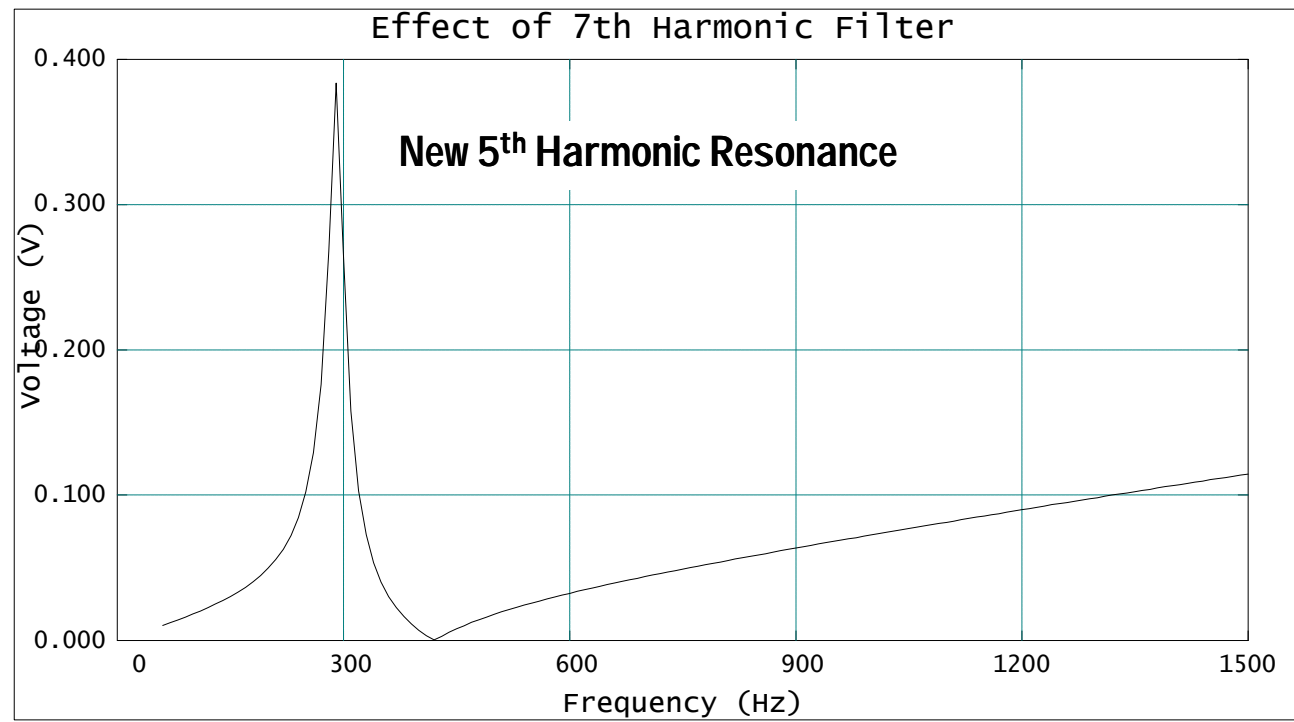


Final Solution

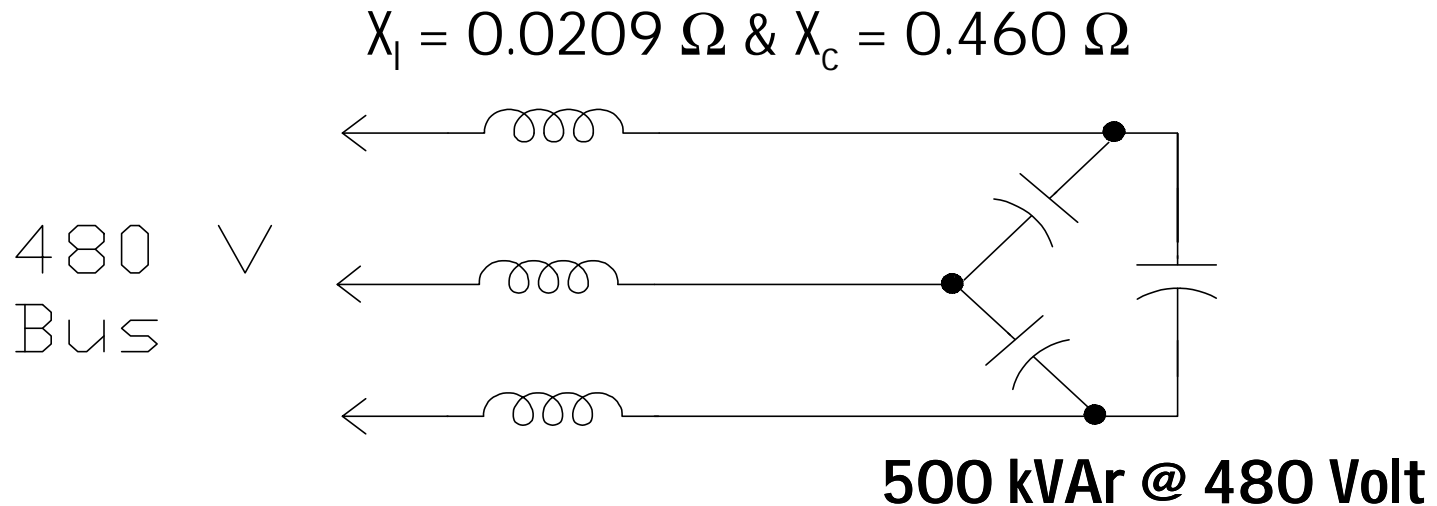- ❑ In general, it is best to apply the filter at or below the lowest harmonic of concern.
- ❑ In this case, a 5th harmonic filter, tuned to 4.7, reduces the 480 volt bus voltage distortion to 2.13%.
- ❑ The filter connections are shown below:



Industrial Tech Brief Case Study

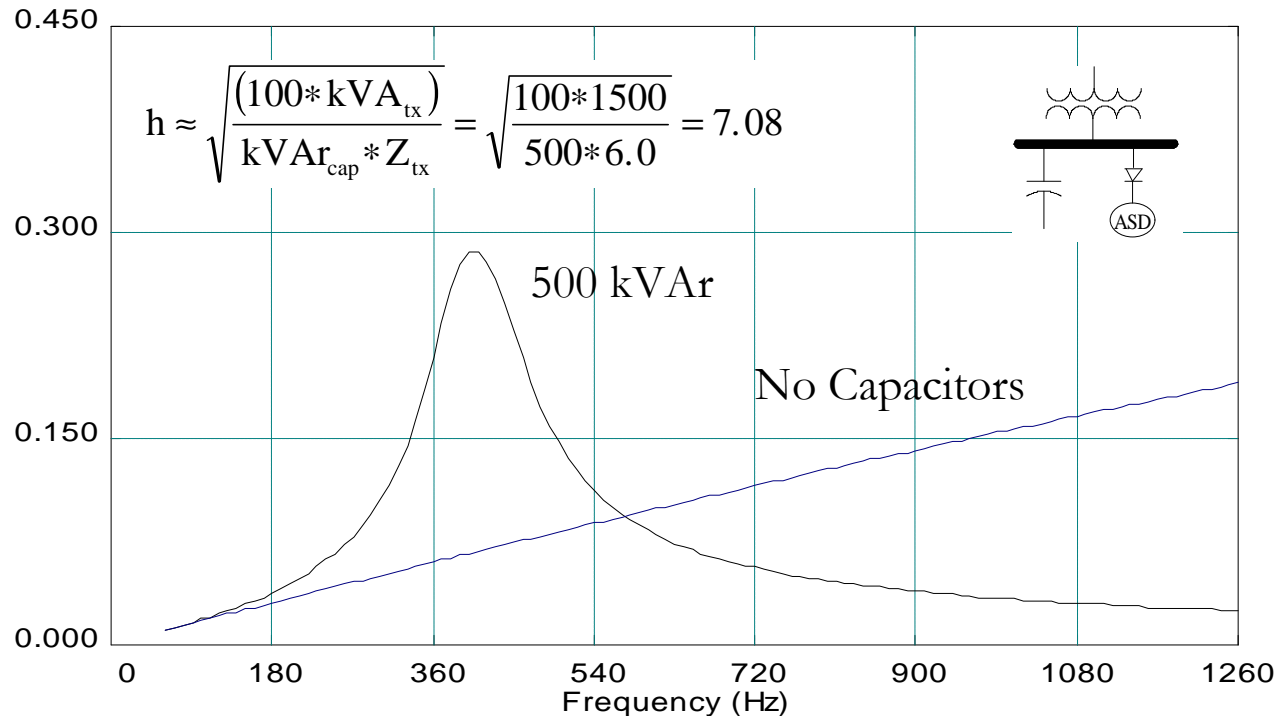□ Preliminary Analysis / Model Development




Industrial Tech Brief Case Study - cont

- ❑ Performing Harmonic Measurements
 - ❑ Determine harmonic source characteristics
 - Waveform
 - Spectrum
 - ❑ Verify harmonic simulation model
 - Use current spectrum from measurement
 - Compare simulated and measured voltage distortion levels
 - ❑ Statistical Characteristics

Industrial Tech Brief Case Study - cont

□ Performing Simulations

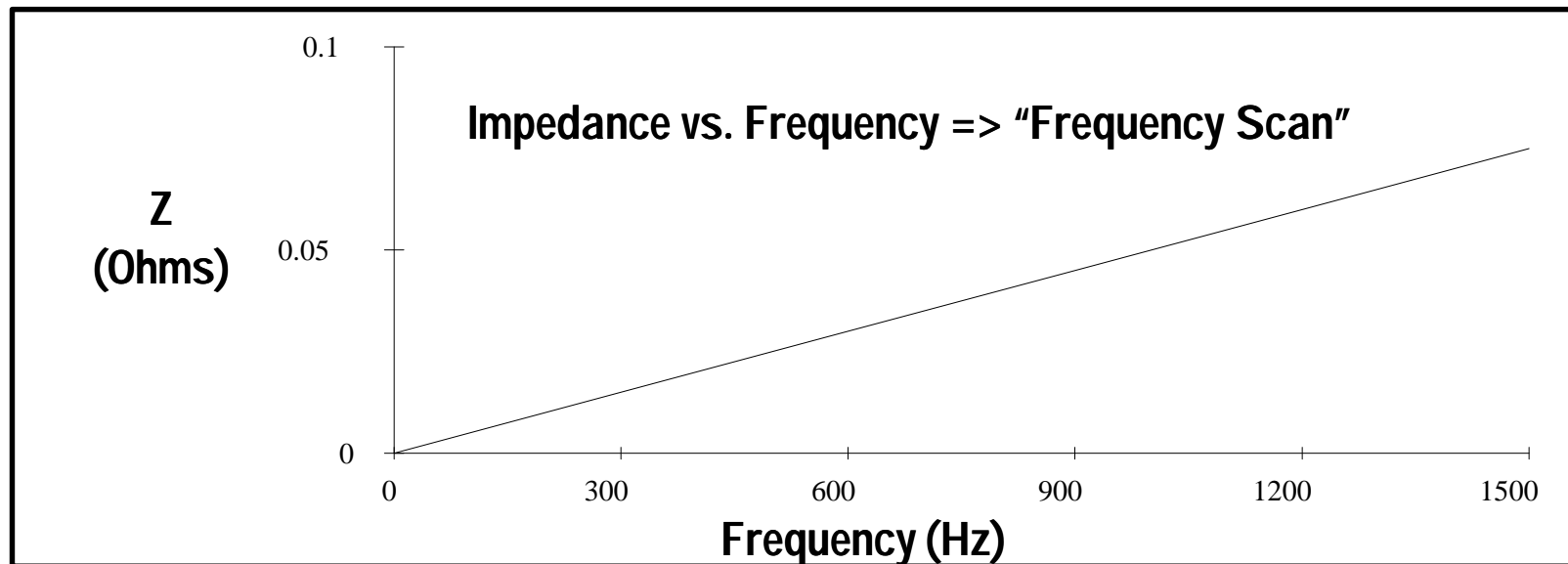

SuperHarm Data File

```
//  
//      File Name:  HARMTECH.SHA  
//  
//      HarmFlo+ Case Study Workbook - Volume #3, Draft #1  
//  
//      Case Study for EPRI Harmonic Tech Brief  
//      Investigation of harmonic concerns in industrial plants  
//  
//      This model is a three-phase representation of the power  
//      system.  
//      All values are in three-phase quantities.  
//  
TITLE          TITLE1 = "Harmonics Tech Brief Case Study"  
              TITLE2 = "HarmFlo+ Case Study Workbook - Volume 3"
```


Industrial Tech Brief Case Study - cont

□ System Parameters

- 12.5kV Source Strength: 200 MVA (0.78Ω)
- 12.5kV Capacitor Size: 3 MVAr
- 12.5kV Feeder Load: 5 MW
- Distribution Feeder Impedance: 0.2Ω

SuperHarm Data File - cont

```
//      Miscellaneous load on 12.5kV Substation Bus
//      Using the Linear Load model
//      5000 kVA of load.  1660 kVA of single phase load.
```

```
LINEARLOAD      NAME = SUBL1A
                 FROM = 12_5A      TO = GROUND
                 KV = 7.216         KVA = 1660
                 DF = 0.90         %PARALLEL = 100.0
```

```
LINEARLOAD      NAME = SUBL1B
                 FROM = 12_5C      TO = GROUND
                 KV = 7.216         KVA = 1660
                 DF = 0.90         %PARALLEL = 100.0
```

```
LINEARLOAD      NAME = SUBL1C
                 FROM = 12_5C      TO = GROUND
                 KV = 7.216         KVA = 1660
                 DF = 0.90         %PARALLEL = 100.0
```


Industrial Tech Brief Case Study - cont

□ Plant Load Summary

- Fluorescent Lighting (THD=21.7%): 200 kVA
- dc Drive (THD=35.2%): 250 HP
- PWM ASD - no choke (THD=130.7%) 25 HP
- PWM ASD - 3% choke (THD=45.1%) 100 HP

SuperHarm Data File - cont

```
//  
//      250 kVAr, 480 Volt Power Factor Correction Capacitor Bank  
//      Installed on 480 Volt Bus #2  
//
```

```
CAPACITOR      NAME = PFCAP2A  
                FROM = 4802A      TO = GROUND  
                KV = 0.277        MVA = 0.06667
```

```
CAPACITOR      NAME = PFCAP2B  
                FROM = 4802B      TO = GROUND  
                KV = 0.277        MVA = 0.06667
```

```
CAPACITOR      NAME = PFCAP2C  
                FROM = 4802C      TO = GROUND  
                KV = 0.277        MVA = 0.06667
```

Industrial Tech Brief Case Study - cont

Harmonic Current Evaluation - Case #1 - (basecase, no power factor correction)

	5 th	7 th	11 th	13 th	17 th	19 th	23 rd	25 th	TDD
519	5.4	5.4	2.5	2.5	2.5	2.3	0.9	0.9	6.8
Actual	3.1	1.3	0.9	0.5	0.5	0.2	0.4	0.1	4.2
Exceed	No	No	No	No	No	No	No	No	No

Harmonic Current Evaluation - Case #2 - (with 200 kVAr power factor correction)

	5 th	7 th	11 th	13 th	17 th	19 th	23 rd	25 th	TDD
519	5.4	5.4	2.5	2.5	2.5	2.3	0.9	0.9	6.8
Actual	4.1	2.4	2.9	0.8	0.3	0.1	0.1	0.1	5.3
Exceed	No	No	Yes	No	No	No	No	No	No

Harmonic Current Evaluation - Case #3 - (with 200 kVAr, 4.7th harmonic filters)

	5 th	7 th	11 th	13 th	17 th	19 th	23 rd	25 th	TDD
519	5.4	5.4	2.5	2.5	2.5	2.3	0.9	0.9	6.8
Actual	1.1	0.9	0.7	0.4	0.4	0.2	0.3	0.1	2.9
Exceed	No	No	No	No	No	No	No	No	No

SuperHarm Data File - cont

```
//      200 kVAr, 480 Volt 4.7th Harmonic Filter
//      Installed on 480 Volt Bus #2

SERIESFILTER      NAME = FILT2A
                   CAPBUS = 4802A           MIDBUS = REACT2A
                   INDBUS = GROUND
                   KV = 0.277           MVA = 0.0667           HARMONIC = 4.7

SERIESFILTER      NAME = FILT2B
                   CAPBUS = 4802B           MIDBUS = REACT2B
                   INDBUS = GROUND
                   KV = 0.277           MVA = 0.0667           HARMONIC = 4.7

SERIESFILTER      NAME = FILT2C
                   CAPBUS = 4802C           MIDBUS = REACT2C
                   INDBUS = GROUND
                   KV = 0.277           MVA = 0.0667           HARMONIC = 4.7
```