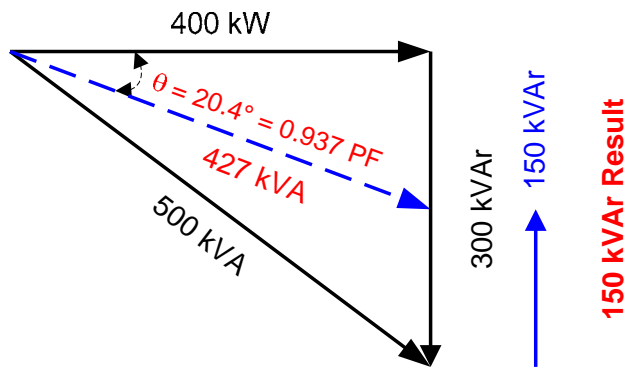


# Understanding Power Factor Correction





**300 kVAR required by loads**  
**150 kVAR power factor capacitor added**  
**150 kVAR result**

$$\text{kVA}_{\text{new}} = \sqrt{(400^2 + 150^2)} = 427 \text{ kVA}$$

$$\text{PF} = \frac{400}{427} \times 100 = 93.7\%$$
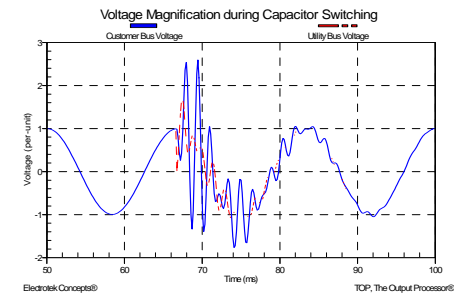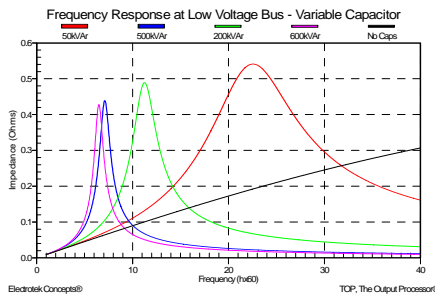
$$\theta = \text{COS}^{-1}(\text{PF}) = \text{COS}^{-1}(0.937) = 20.4^\circ$$



**April 26, 2005**

**Thomas Grebe**  
**Electrotek Concepts, Inc.**

# Introduction

---

- ◆ Definition of power factor
- ◆ Benefits of improving power factor
- ◆ Methods for improving power factor
- ◆ Determining financial savings
- ◆ Customer/utility application considerations:
  - Harmonic resonances
  - Transient overvoltages


# Power Factor Definition

---


- ◆ Power factor measures how effectively electrical power capacity is being used.
- ◆ Related to power flow in electrical systems:
  - ***Real Power*** (a.k.a. active or working power) is the power that is converted into useful work for creating heat, light, and motion. Measured in kW, totalized in kWh.
  - ***Reactive Power*** (a.k.a. magnetizing power) is the power that sustains an electromagnetic field in inductive and capacitive equipment. Measured in kVAr, totalized in kVArh.
  - ***Total Power*** (a.k.a. apparent power) is the combination of real and reactive power. Measured in kVA, totalized in kVAh.

# Illustrated using Power Triangle

---

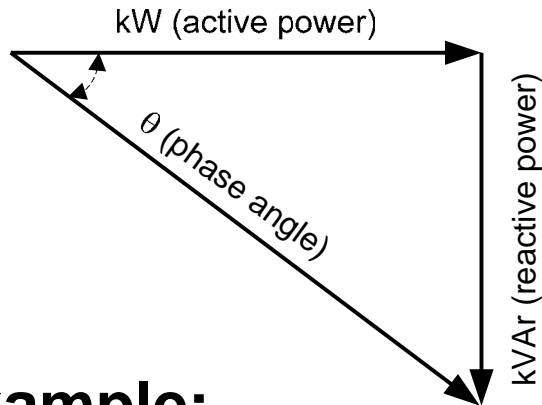

**Example:**

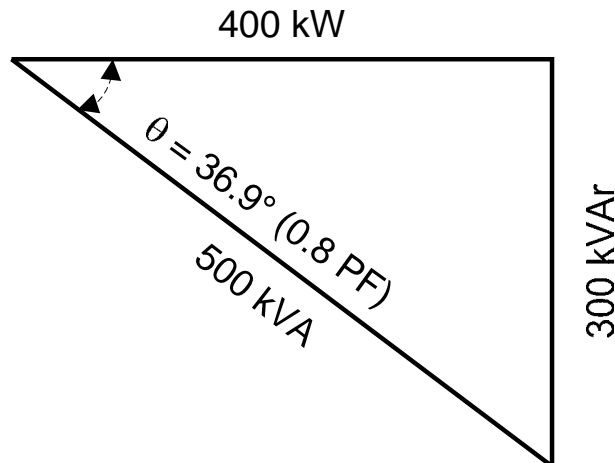

$$\text{Power Factor} = \frac{\text{Active Power (kW)}}{\text{Apparent Power (kVA)}}$$

$$\text{kVA} = \sqrt{(\text{kW}^2 + \text{kVAR}^2)} = \sqrt{(400^2 + 300^2)} = 500\text{kVA}$$

$$\text{PF} = \frac{\text{kW}}{\text{kVA}} (\text{x100 for percent}) = \frac{400}{500} \times 100 = 80\%$$

$$\theta = \text{COS}^{-1}(\text{PF}) = \text{COS}^{-1}(0.80) = 36.9^\circ$$

# Displacement vs. True Power Factor

---


- ◆ Harmonic distortion in the voltage and/or current changes the way power factor should be calculated.
- ◆ True power factor (TPF) is defined as the ratio of real power to the total volt-amperes in the circuit:

$$\text{DPF} = \text{Cos}\theta = \frac{\text{kW}}{\text{kVA}}$$

$$\text{TPF} = \frac{\text{Power}_{\text{real}}}{\text{Voltamperes}_{\text{total}}} = \frac{P}{V_{\text{RMS}} * I_{\text{RMS}}} \approx \sqrt{\frac{1}{(1 + \text{THD}_{\text{current}}^2)}}$$

# True Power Factor Example

- ◆ Sample ASD current waveform:

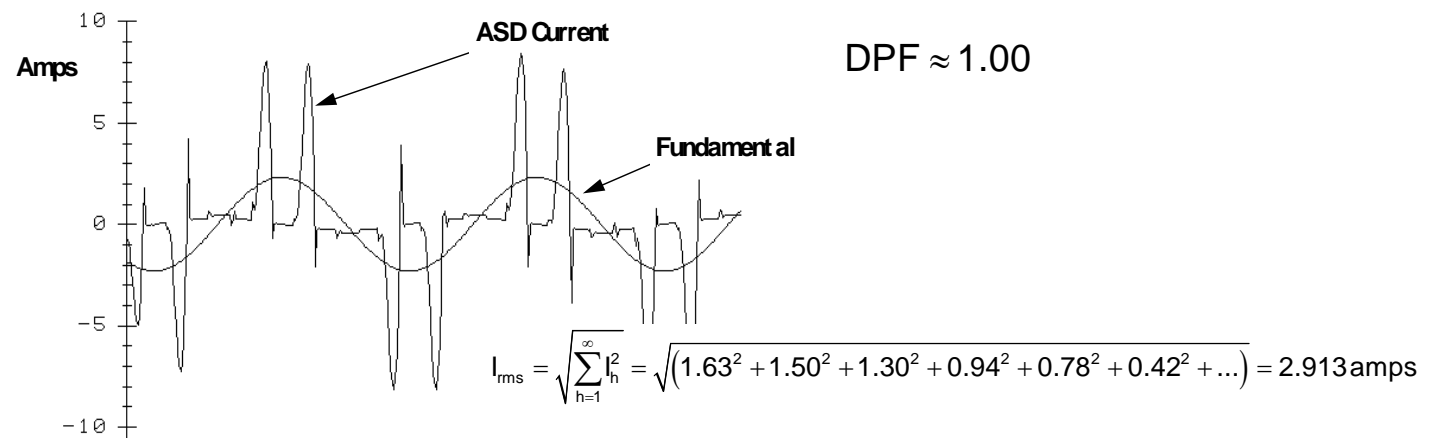

$$P = V_1 * I_1 * \cos\theta = (480V)(1.63A)(1) = 782.4W$$

$$TPF = \frac{\text{Power}_{real}}{\text{Voltamperes}_{total}} = \frac{P}{V_{RMS} * I_{RMS}} = \frac{782.4W}{(480V)(2.913A)} = 0.559 \approx 56\%$$

$$TPF \approx \sqrt{\frac{1}{(1 + 1.48^2)}} = 0.559 \approx 56\%$$

# Typical Equipment Power Factor

---

<b>Equipment Description</b>	<b>Typical Displacement Power Factor (%)</b>
<b>Induction Motors</b>	<b>70-80</b>
<b>Diode Rectifiers (small ASDs)</b>	<b>95-90</b>
<b>Fluorescent Lighting: Standard Ballast (also HID)</b>	<b>70</b>
<b>Electronic Ballast</b>	<b>90</b>
<b>Phase Controlled Rectifier (dc &amp; large ac drives)</b>	<b>40-90</b>
<b>Arc Furnaces</b>	<b>75-90</b>
<b>Arc Welding</b>	<b>35-60</b>
<b>Resistance Welding</b>	<b>40-60</b>

# Benefits of Improving Power Factor

---

- ◆ The principle benefit is usually lower monthly electric bills.
- ◆ Additional benefits:
  - More efficient use of the electrical system
  - Improved voltage regulation due to reduced line voltage drop
  - Increased load carrying capabilities in existing circuits
  - Possible reduction in size of transformers, cables, and switchgear for new installations
  - Reduced power system losses



# Methods for Improving Power Factor

---

- ◆ Improving power factor by reducing reactive power requires equipment that operates at a leading power factor.
- ◆ Options include:
  - Static capacitors – devices without moving parts that provide magnetizing current to the load.
  - Synchronous motors – either over-excited or under-loaded motors with full excitation will supply kilovars to the system.
  - Power electronic devices – (e.g., SVC) that can provide reactive power and harmonic compensation.
  - Capacitors are generally the most economical option for reactive compensation.

# Applying Capacitors

---

- ◆ Capacitors are generally the most economical source of reactive compensation. Other advantages include:
  - low losses (less than  $\frac{1}{4}$  watt/kVAr)
  - essentially no maintenance
  - light, compact units which can be combined as needed, make capacitors relatively easy to install and modify as reactive compensation needs change

# Capacitor Bank Sizing

---

- ◆ The rating of the power factor correction capacitor required to correct a load to a desired power factor is often approximated using the following approach:

$$\text{kVAr} = \text{kW} * \left( \tan \phi_{\text{original}} - \tan \phi_{\text{desired}} \right)$$


where:

- kVAr = required compensation in kVAr
- kW = real power in kW
- $\tan \phi_{\text{original}}$  = original power factor phase angle
- $\tan \phi_{\text{desired}}$  = desired power factor phase angle

Orig PF	Corrected Power Factor										
	0.80	0.82	0.84	0.86	0.88	0.90	0.92	0.94	0.96	0.98	1.00
0.50	0.982	1.034	1.086	1.139	1.192	1.248	1.306	1.369	1.440	1.529	1.732
0.52	0.893	0.945	0.997	1.049	1.103	1.158	1.217	1.280	1.351	1.440	1.643
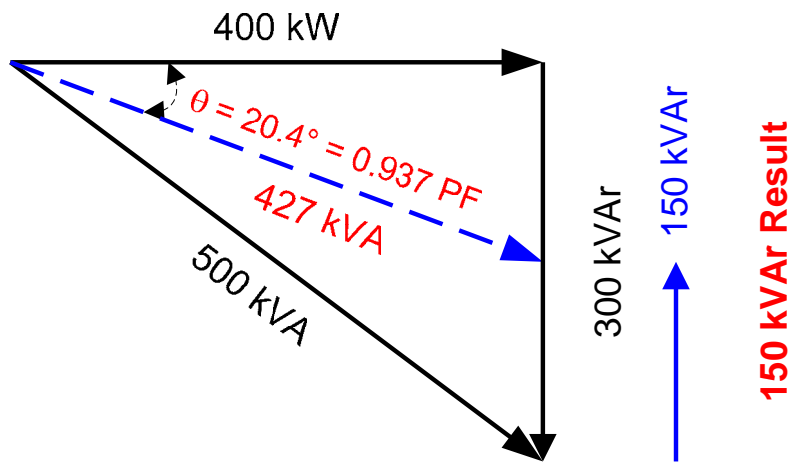
# Illustrated using Power Triangle

- ◆ Power factor correction capacitors supply the necessary reactive portion of power (kVAr) for inductive devices. By supplying its own source of reactive power, a facility frees the utility from having to supply it.



**300 kVAr required by loads**

**150 kVAr power factor capacitor added**


**150 kVAr result**

$$\text{kVA}_{\text{new}} = \sqrt{(400^2 + 150^2)} = 427 \text{ kVA}$$

$$\text{PF} = \frac{400}{427} \times 100 = 93.7\%$$

$$\theta = \text{COS}^{-1}(\text{PF}) = \text{COS}^{-1}(0.937) = 20.4^\circ$$
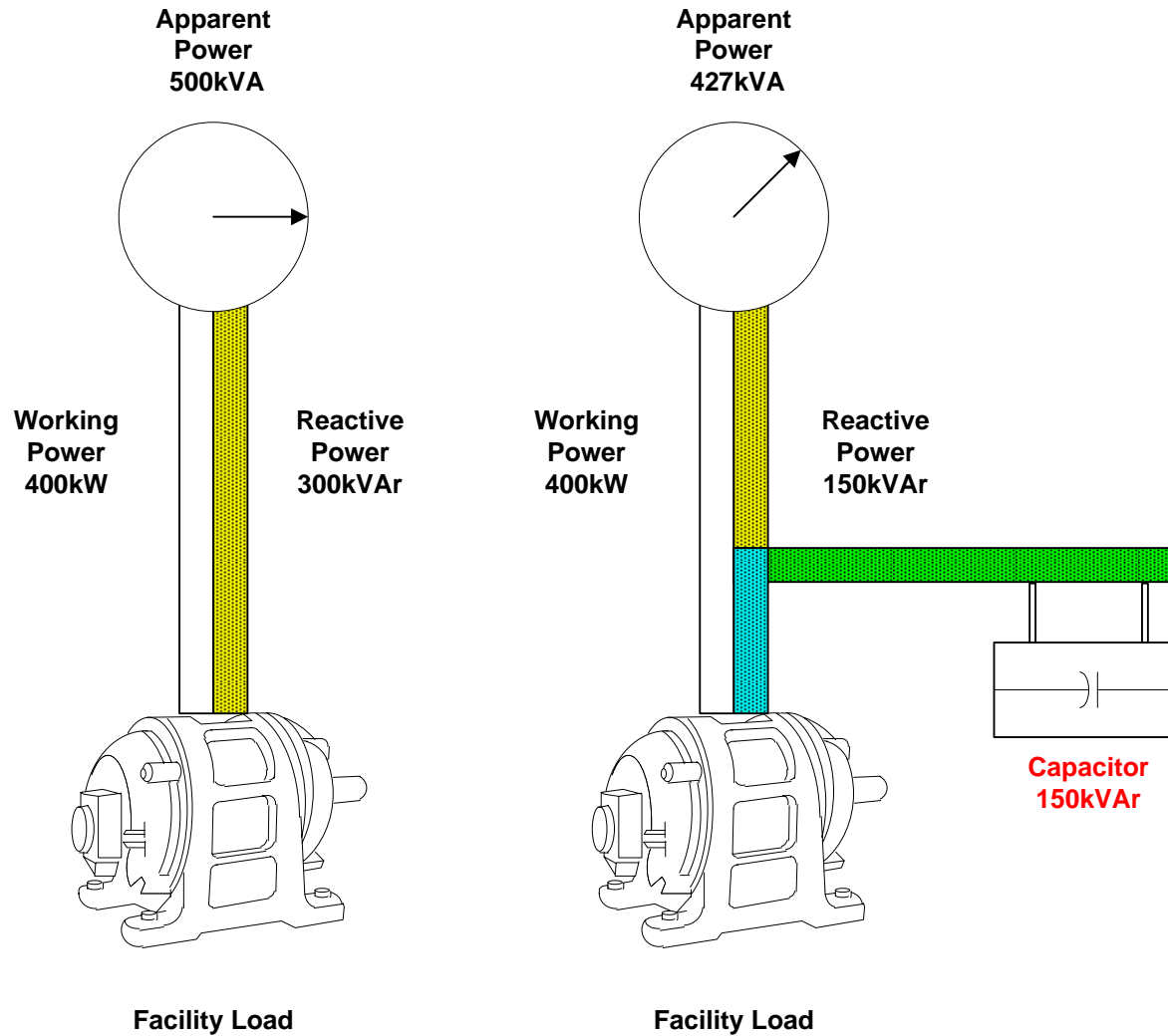
# Illustration of Power Factor Correction




# Capacitor Bank Control

- ◆ Power factor correction capacitor banks are either switched or fixed. Generally, in determining the type of capacitor bank required, the following guidelines should be considered:
  - Fixed capacitor banks are sized for the minimum load conditions.
  - Switched capacitor banks are designed for load levels above the minimum condition up to peak load.

Switching based on:

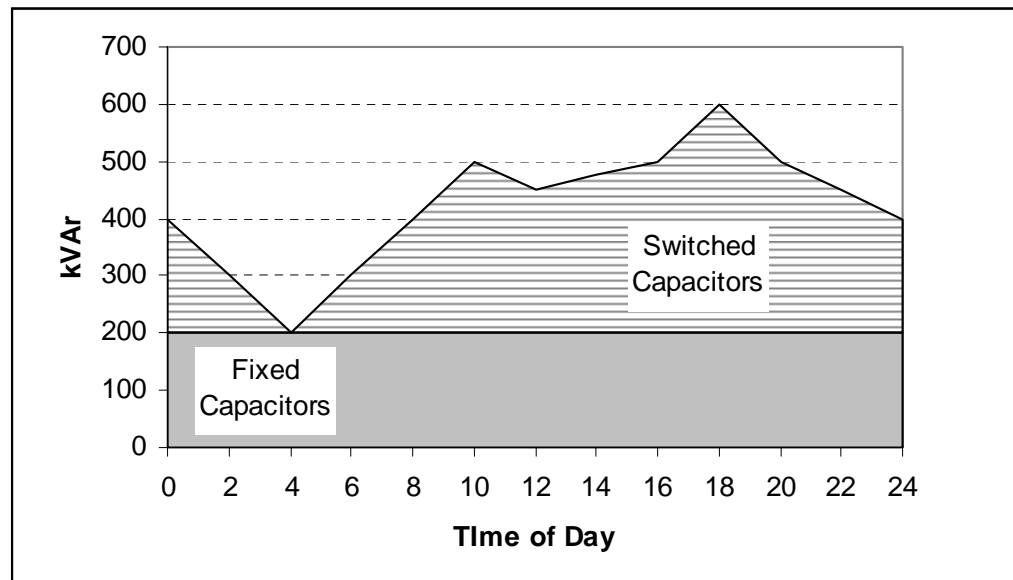- Voltage
- Current
- Var or reactive current
- Time
- Temperature



# Utility Power Factor Rates

---

- ◆ Each utility has their own method and related rates for determining power factor penalties.
- ◆ Number of methods for charging for poor power factor, including:
  - Charges for kVArh
  - Charges for kVAr demand
  - Charges for kVA demand
  - Charges for adjusted kW demand
  - Charges based on a percentage of the demand or base charge

# Determining Payback

---

- ◆ Electric bills will include an additional surcharge if the rate schedule has a power factor penalty.
- ◆ This penalty can be reduced or eliminated with the proper application of power factor correction capacitors.
- ◆ The savings realized needs be weighed against the equipment, installation, and maintenance costs to determine if the payback time is acceptable.
- ◆ Payback times can vary significantly due to wide range of utility power factor penalties and equipment costs.
- ◆ A reasonable range for payback period might be between 6 months and 2 years.



# Example Payback Case

---

- ◆ A facility with an **800 kW** load has a demand of **1000 kVA**. The utility has a demand charge of **\$2.50/kVA** for customers with power factors below **95%**.
- ◆ The present power factor may be determined using:  
**Power Factor = kW/kVA = 800kW/1000kVA = 0.80 or 80%**
- ◆ The amount of power factor correction capacitors that are required to improve the power factor to **95%** may be determined using:

$$\begin{aligned} \text{kVAr} &= \text{kW} * (\tan \phi_{\text{original}} - \tan \phi_{\text{desired}}) \\ &= 800\text{kW} * (\tan(\cos^{-1} 0.80) - \tan(\cos^{-1} 0.95)) = 337\text{kVAr (use 360kVAr)} \end{aligned}$$

## Payback Case - continued


---

- ◆ The new kVA demand after the capacitors have been installed may be determined using:  
$$\text{kVA} = \text{kW}/\text{power factor} = 800/0.95 = 842 \text{ kVA}$$
- ◆ The annual savings may be determined using:  
$$\begin{aligned} (1000 \text{ kVA} - 842 \text{ kVA}) * \$2.50/\text{kVA} &= \$395/\text{month} * \\ 12 \text{ months} &= \$4,740 \end{aligned}$$
- ◆ The cost to purchase and install 360 kVAr of capacitors (cost assumed to be \$15/kVAr):  
$$360 \text{ kVAr} * \$15/\text{kVAr} = \$5,400$$
- ◆ The payback period for the capacitor installation may be determined using:  
$$\$5,400/\$4,740 = 1.14 \text{ (or about 14 months)}$$

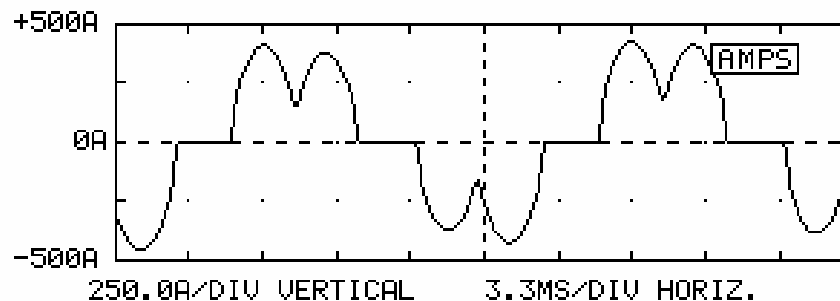
# Harmonic Problems

---


- ◆ Harmonics can cause equipment to misoperate, capacitor banks to fail, transformers to overheat, or breakers to trip mysteriously.
- ◆ Capacitors create resonances that can increase distortion levels significantly.



# Frequency Response – Resonance

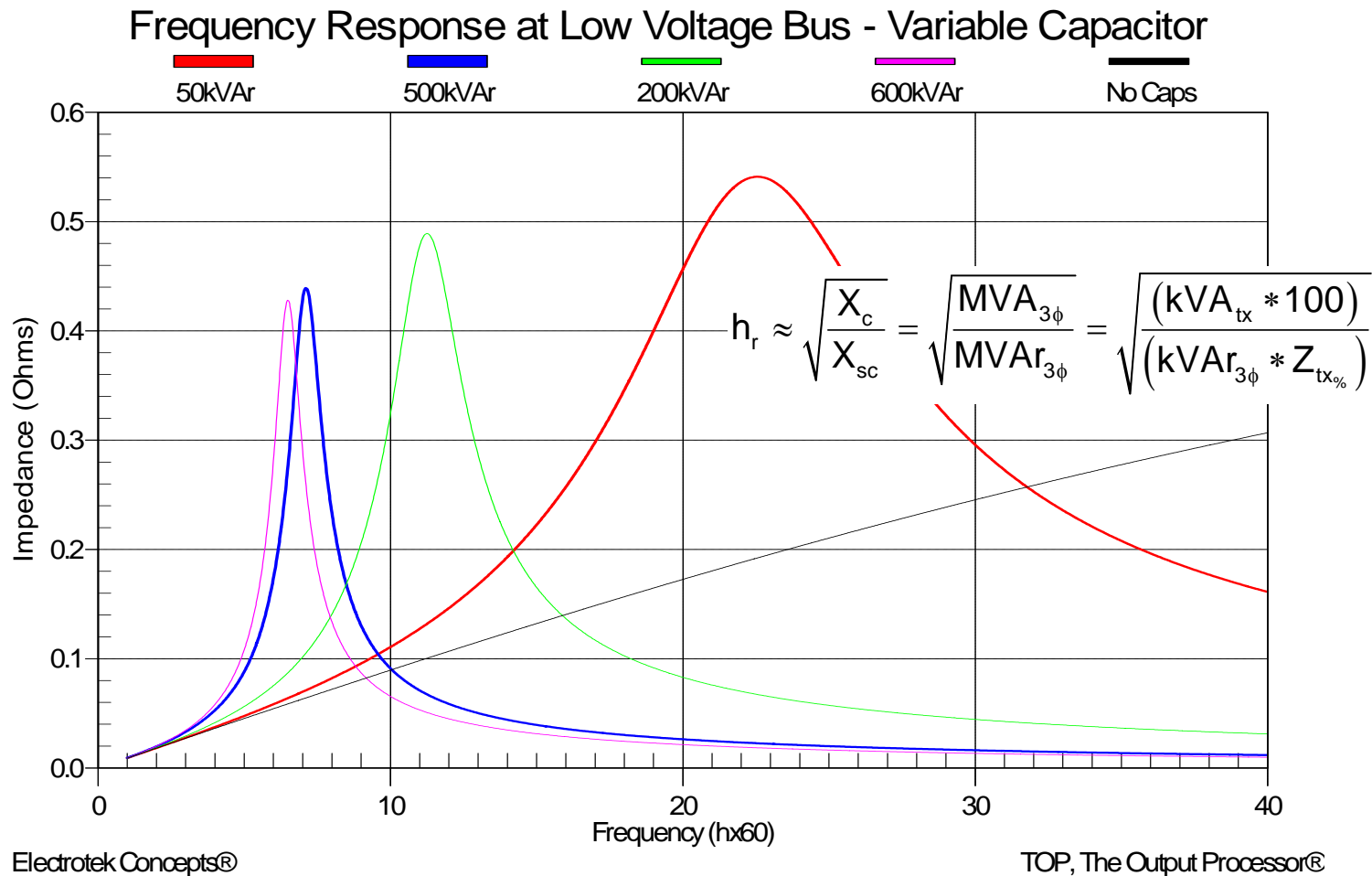

# Applying Capacitors as Filters

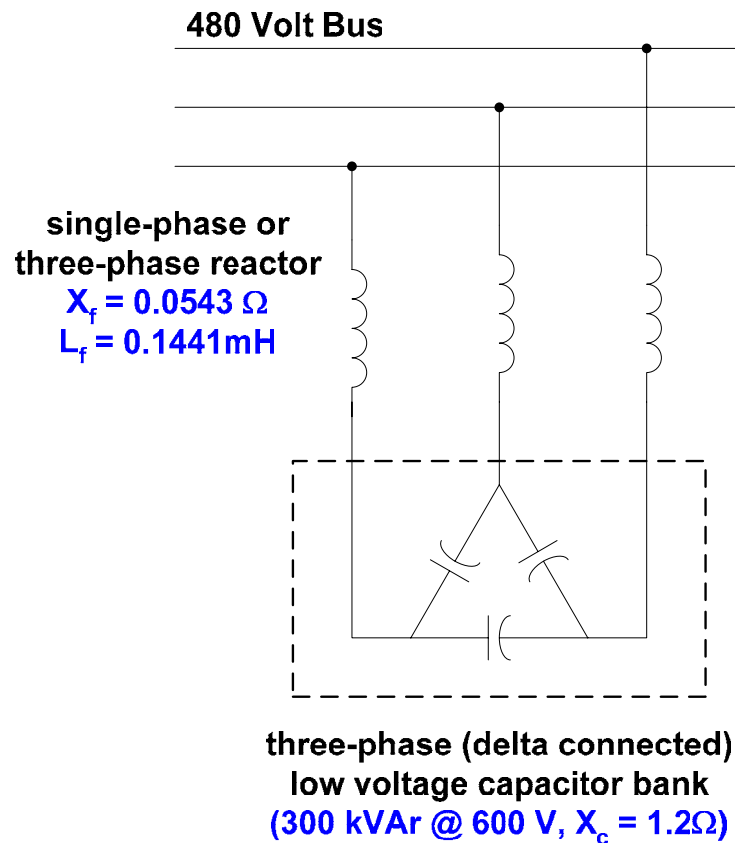

$$X_c = \frac{\text{kV}_{\text{cap}}^2}{\text{MVAR}_{\text{cap}}} = \frac{\left(\frac{\text{V}_{\text{cap}}}{1000}\right)^2}{\left(\frac{\text{kVAR}_{\text{cap}}}{1000}\right)} = \frac{\left(\frac{600}{1000}\right)^2}{\left(\frac{300}{1000}\right)} = 1.2\Omega$$

$$X_f = \frac{X_c}{n^2} = \frac{1.2}{4.7^2} = 0.0543\Omega$$

$$L_f = \frac{X_f}{(2\pi * f_{\text{system}})} = \frac{0.0543\Omega}{(2\pi * 60)} = 0.1441\text{mH}$$

where:

$X_c$  = capacitive reactance of power factor correction capacitor


$X_f$  = inductive reactance of series reactor

$L_f$  = inductance of series reactor

$n$  = tuning harmonic (multiple of  $f_{\text{system}}$ )

$f_{\text{system}}$  = system frequency

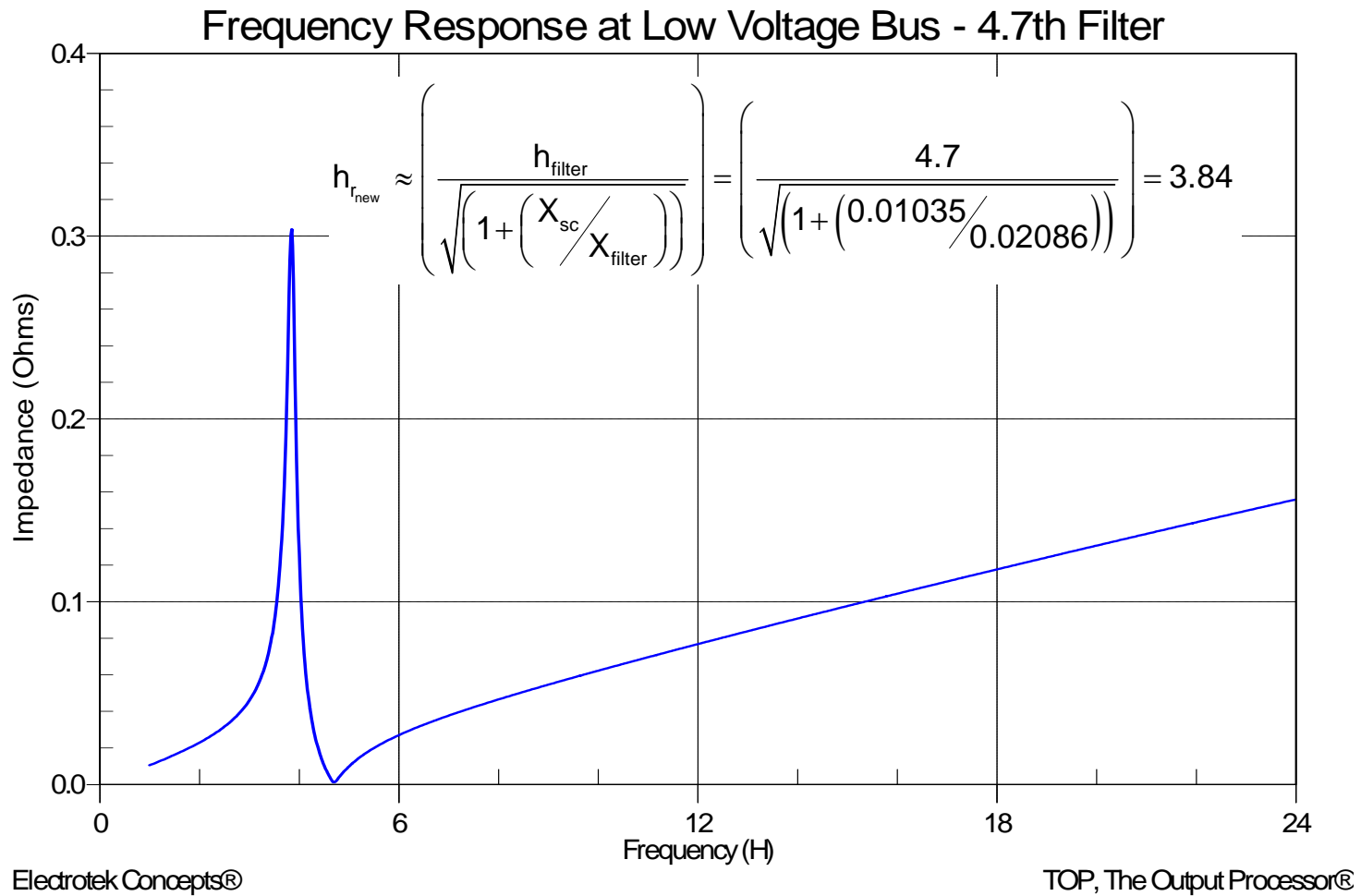
# Solution to Resonance Problem – Filters



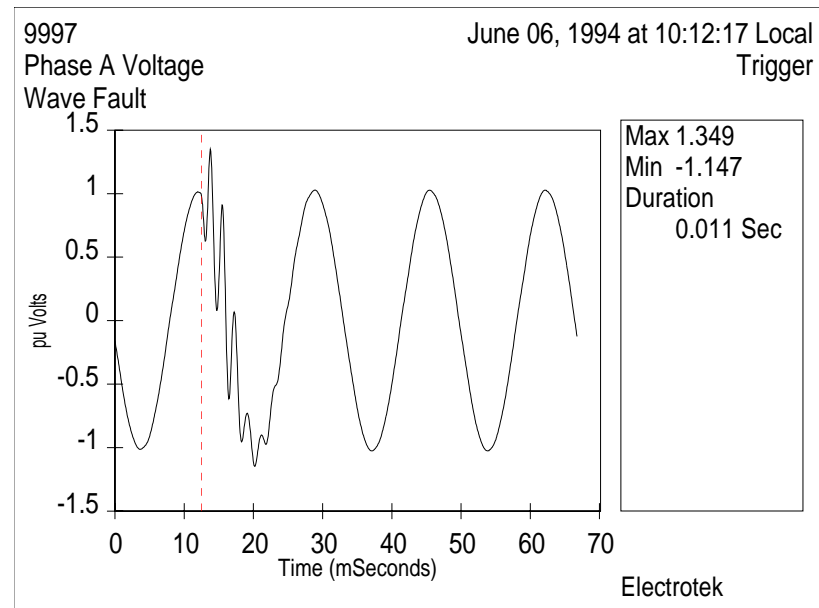
# Transient Problems

---

- ◆ Utility capacitor switching produces transient voltages that:
  - can be magnified in a customer facility that has power factor correction capacitors (*voltage magnification*)
  - can cause nuisance tripping of power electronic-based devices (e.g., ASDs).




# Voltage Magnification Circuit

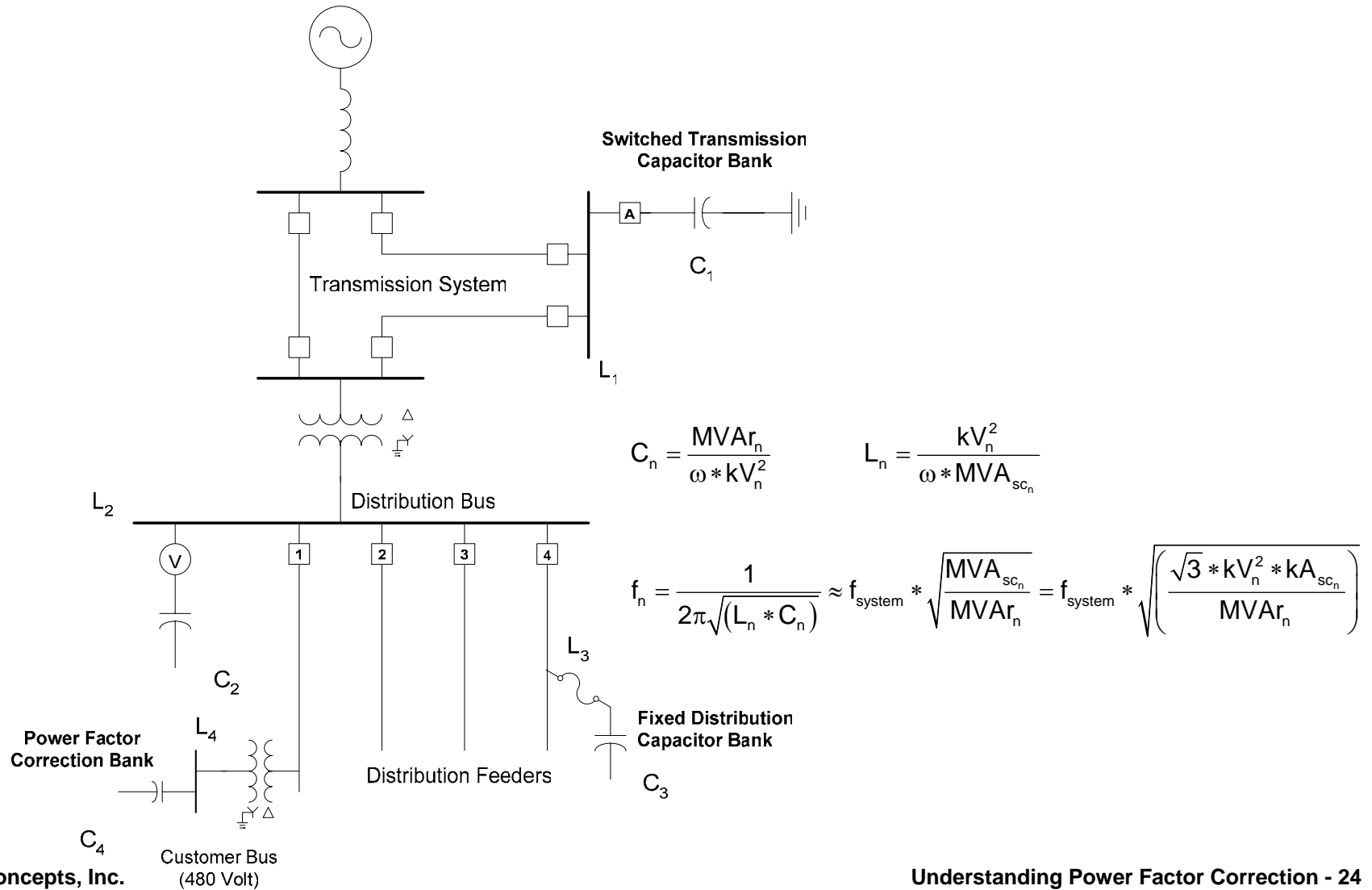



# Example Transient Voltage Waveform

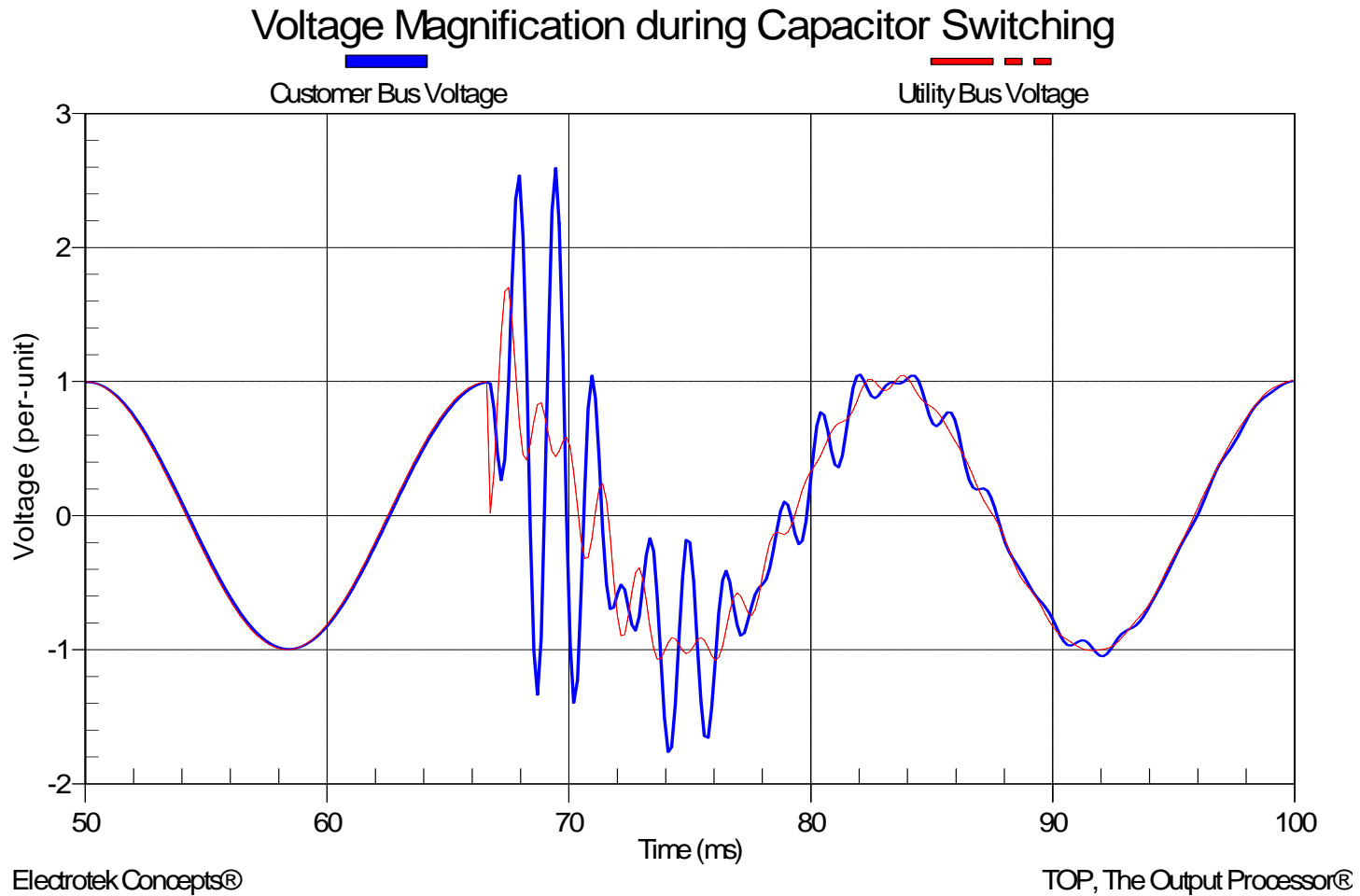

# Solutions to Transient Problems

---

- ◆ Solutions to the voltage magnification and nuisance tripping generally involve:
  - Using an overvoltage control method, such as pre-insertion resistors or synchronous closing control.
  - Detuning the circuit by changing capacitor bank sizes, moving banks, and/or removing banks from service.
  - Switching large banks in more than one section.
  - Applying surge arresters (MOVs) at the remote location.
  - Converting the customer's power factor correction banks into harmonic filters.
  - Adding series inductors (chokes) on the input of adjustable speed drives.

# Additional Information

---

- ◆ Electrotek provides consulting services related to power factor, transient, and harmonic studies using tools such as PSCAD, and SuperHarm.
- ◆ Additional Information:
  - Electrotek (studies, training, and seminars):  
<http://www.electrotek.com/>
  - PQSoft (simulation and analysis tools and support):  
<http://www.pqsoft.com/>
  - Monitoring service:  
<http://www.powermonitoring.com/>